

CS4341 Digital Logic & Computer Design

Lecture Notes 18

Omar Hamdy


Assistant Professor

Department of Computer Science

Review: Setup and Hold Time Constraints


➤ Setup Time Constraint:

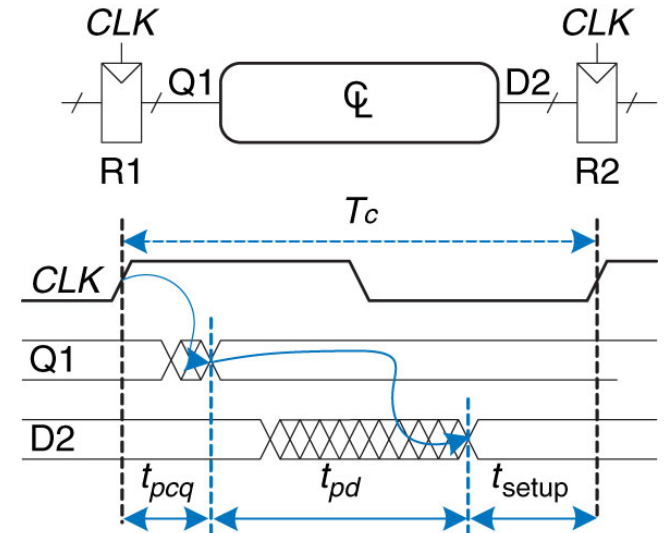- $T_c \geq t_{pcq} + t_{pd} + t_{setup}$
- $t_{pd} \leq T_c - (t_{pcq} + t_{setup})$



➤ Hold Time Constraint:

 
- $t_{ccq} + t_{cd} \geq t_{hold}$
- $t_{cd} \geq t_{hold} - t_{ccq}$



Timing Analysis Example


➤ The shown circuit has the following time specifications:

 - $t_{ccq} = 30$ ps
- $t_{pcq} = 80$ ps
- $t_{setup} = 50$ ps
- $t_{hold} = 60$ ps
- $t_{pd} = 40$ ps
- $t_{cd} = 25$ ps
- What is the maximum clock frequency?
- Is there any hold time violations?





Solution: Critical and Shortest Paths

 - Determine the critical path (sum of all t_{pd} on the longest path)
- Determine the short path (sum of all t_{cd} on the shortest path)




Solution: Critical and Shortest Paths

  

- Calculate $T_c \geq t_{pcq} + 3t_{pd} + t_{setup}$
- $T_c \geq 80 + 3 \times 40 + 50 = 250 \text{ ps}$
- Therefore, maximum clock frequency $f_c = 1/T_c \leq 4 \text{ GHz}$
- For the short path, X' can start changing as early as $t_{ccq} + t_{cd}$
- Hence, X' will start changing as early as $30 + 25 = 55 \text{ ps}$, which violates the flip-flop hold time of 60 ps .


Timing Analysis Example 2

- The buffers in this circuit were added to slow down the short path to fix the hold time violation.
- What is the maximum clock frequency?
- Is there still any hold time violations?
- Solution:
 - Critical path is not affected (why)?
 - Hence, clock frequency is the same ≤ 4 GHz
 - For short path, X' will start changing after $30 + 2 \times 25 = 80$ ps. This is more than the required 60 ps hold time. Therefore, there is no violation in the circuit.

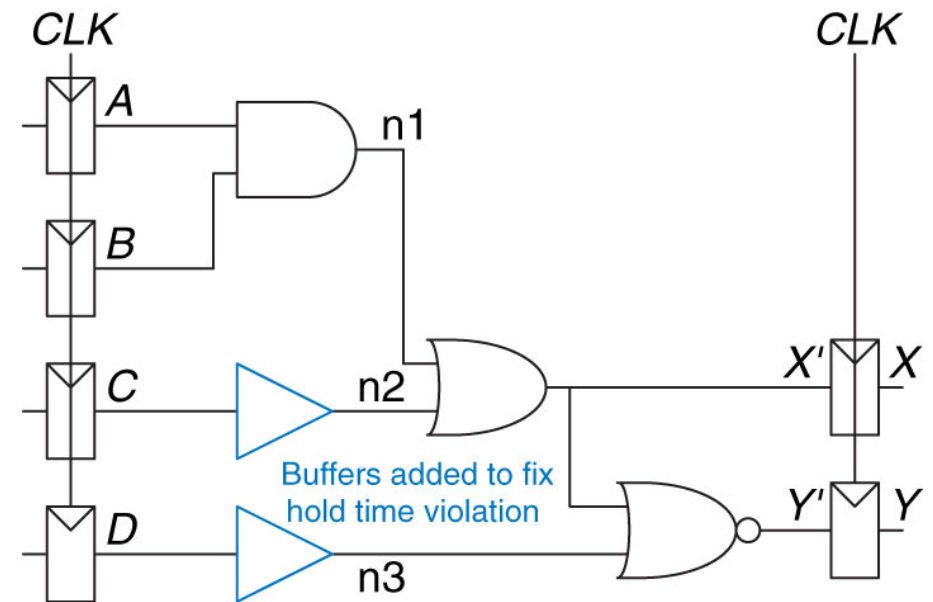



Clock Skew

 - The clock itself can have its own timing problems caused by many reasons.
- Wire length, noise, clock gating, etc
- This variation in clock edges is called clock skew



Clock Skew Time

  - The worst-case clock skew timing must be added to the timing calculations.
- The dark clock line is latest time the clock signal might reach a register. All other lines means the signal might arrive up to t_{skew} earlier





Accounting for Clock Skew

➤ Clock skew needs to be accounted for in T_c , t_{pd} , t_{cd} calculations.

➤ $T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$

➤ $t_{pd} \leq t_c - (t_{pcq} + t_{setup} + t_{skew})$

  ➤ $t_{cd} \geq t_{hold} + t_{skew} - t_{ccq}$




Timing Analysis with Clock Skew Example

- Study the impact of a 50 ps clock skew on the same circuit analysis

➤ Solution

- Critical path and short path remain the same with only calculation difference
- $T_c \geq t_{pcq} + 3 \times t_{pd} + t_{setup} + t_{skew}$
- $T_c \geq 80 + 3 \times 40 + 50 + 50 = 300 \text{ ps}$
- Therefore, $f_c = 1/T_c \leq 3.33 \text{ GHz}$
- t_{cd} is the same as 55 ps, but the hold time is now $60 + 50 = 110 \text{ ps}$. Hence, the hold violation became much worse.
- How can we fix this problem?
 - More buffers, or flip-flops with shorter hold time.

 

Parallelism


- We start with some key definitions:
 - Token: a group of inputs that are processed to produce a group of outputs
 - Latency: The latency of a system is the time required for one token to pass through the system from start to end.
 - Throughput: The throughput is the number of tokens that can be produced per unit time
- How can we increase the system throughput?
 - One method is to try to decrease the latency, so more tokens can be processed per unit time
 - Another method is to try processing multiple tokens at the same time (parallelism)

Parallelism

- Parallelism has two forms:
 - Spatial parallelism: multiple copies of the hardware are provided so that multiple tasks can be done at the same time.
 - Temporal parallelism (pipelining): a task is broken into stages, like an assembly line, and hence multiple tasks can be spread across the stages.
 - Although each task must pass through all stages, a different task will be in each stage at any given time so multiple tasks can overlap.
 - Simple example: assume preparing a tray of cookies (token) requires 5 minutes rolling in the tray and 15 minutes baking. Study the spatial parallelism if we use two ovens and two helpers, vs a temporal parallelism approach.
 - Use 1 hr as the time unit

Parallelism

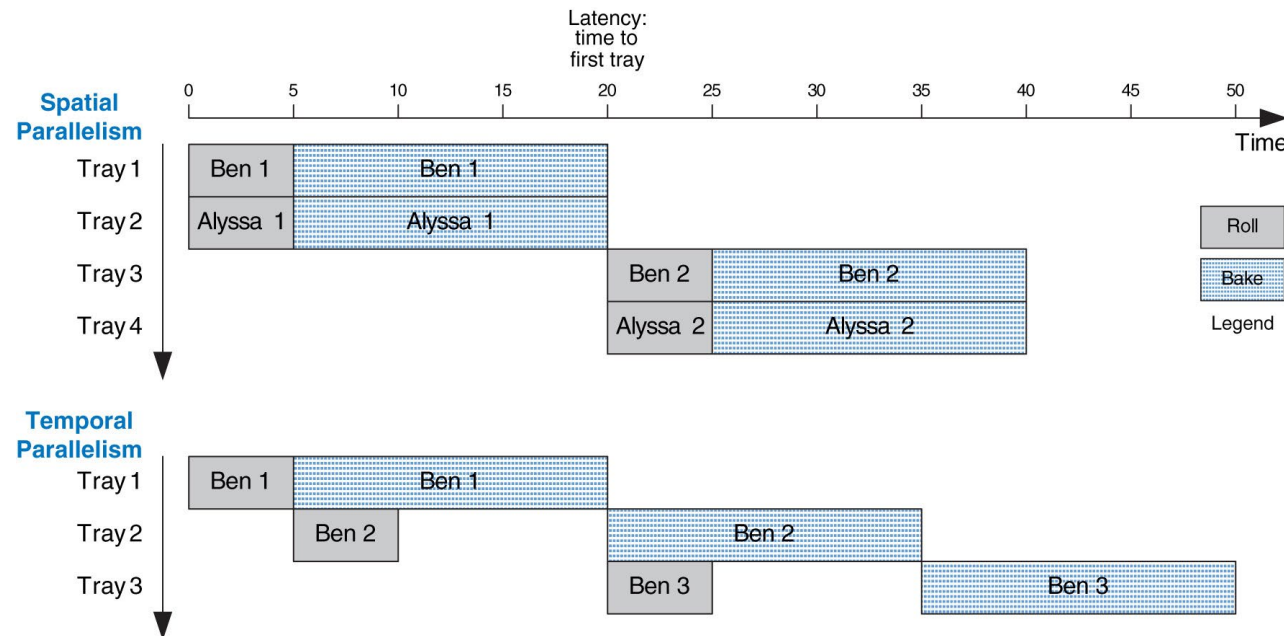- Single process: latency is 1/3 hr and throughput is 3 trays/hr
- Spatial parallelism: Latency is the same, but throughput is double the single process of 6 trays/hr
- Pipelining: Once a tray is put in the oven, work on rolling the next. Latency is the same, and throughput is 4 trays/hr (why)?




Parallelism

- In digital circuits, if a task has latency L , in a single process system, the throughput is $1/L$
- In a spatially parallel system with N copies of the hardware, the throughput is N/L
- In pipelined system, ideally the task is broken into N equal stages, hence throughput is N/L (why)?
- However, it is not practical to assume there will be N equal stages. If the longest step takes L_1 , then the throughput is $1/L_1$ in pipelines system.
- Pipelining is advantageous over spatial parallelism because it can speed up the performance without duplicating the hardware.


Pipelining Implementation

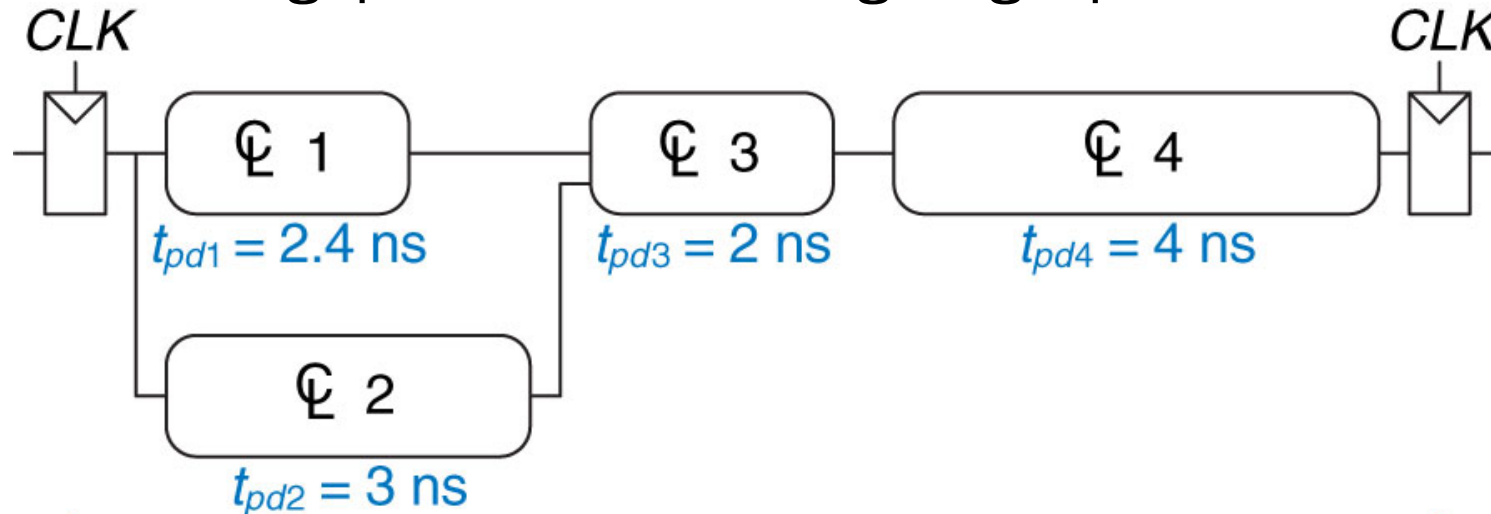- In pipelining, the combinational circuit is divided into smaller stages by insertion of registers.
- Registers are important to prevent tokens from catching up with one another.
- Calculate the throughput of the following single process circuit




Throughput Calculation – No Pipelining

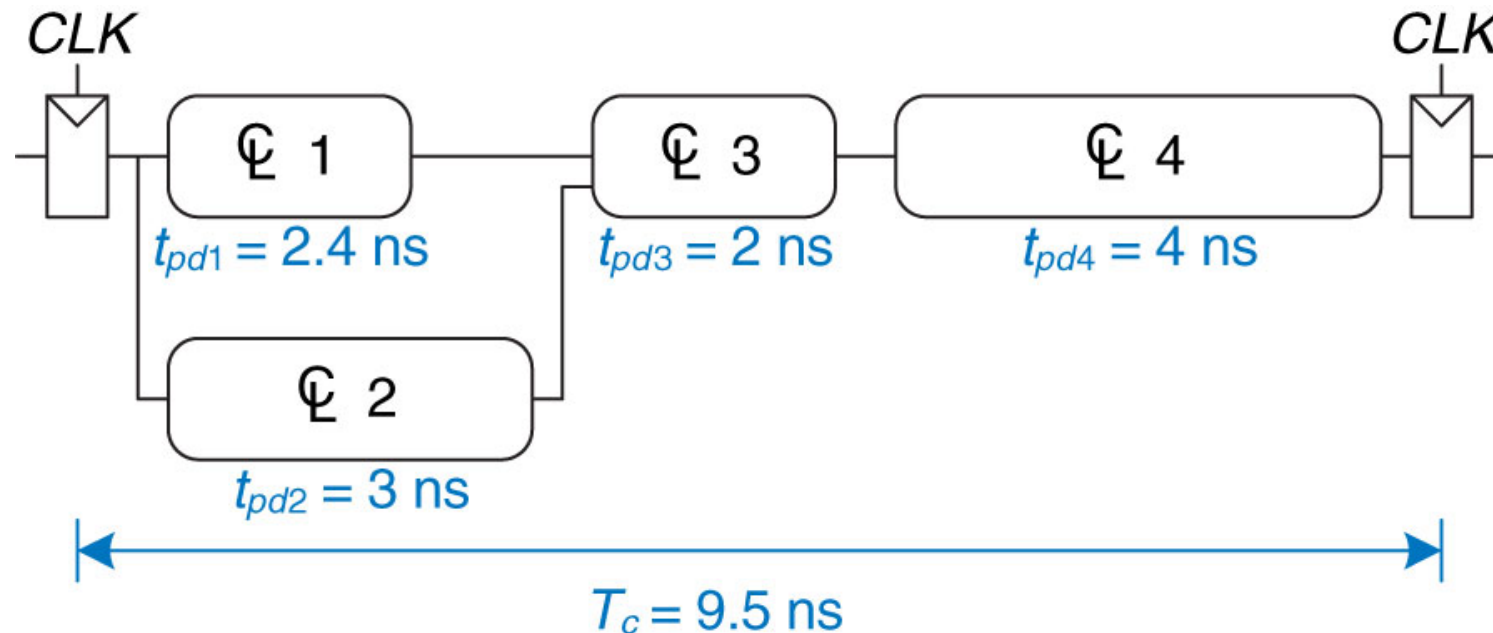- First, we calculate the latency, which is T_c in this circuit (why)?
 - $T_c = t_{pcq} + t_{pd} + t_{setup}$
 - t_{pd} = sum of all t_{pd} on the critical path (CL 2, 3 and 4) = $3 + 2 + 4 = 9$ ns
 - Assume $t_{pcq} = .3$ ns and $t_{setup} = 0.2$ ns
 - $T_c = 9 + .5 = 9.5$ ns → throughput $1/T_c = 105$ MHz




Throughput Calculation – 2 Stage Pipeline

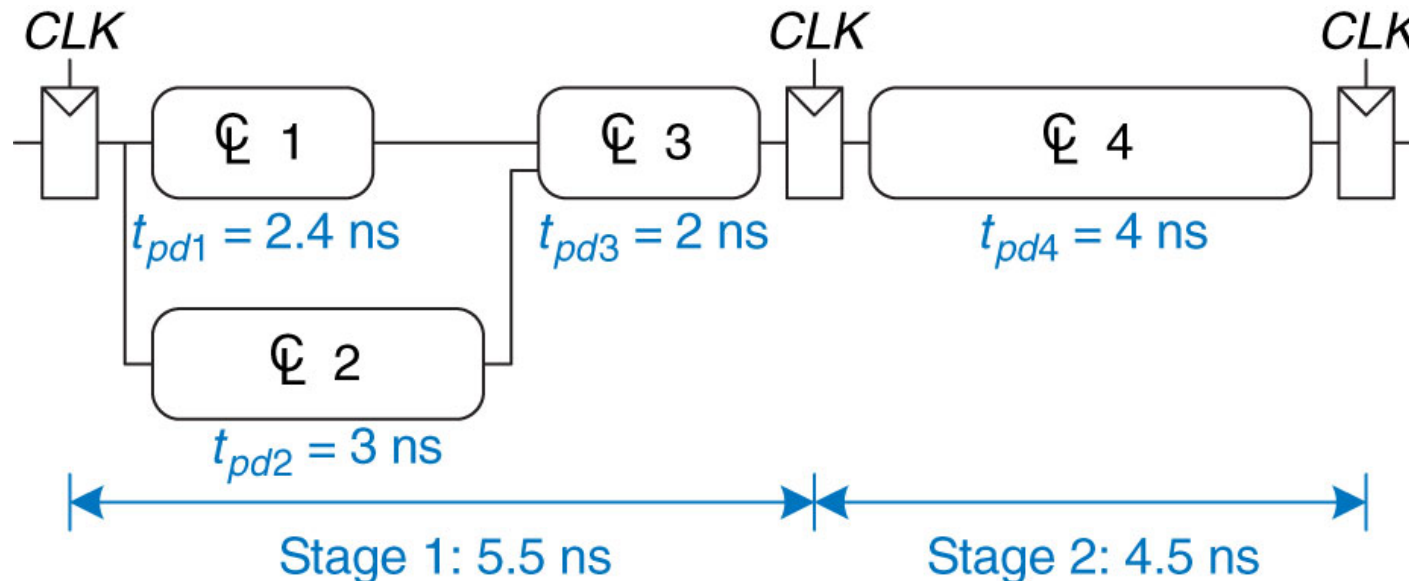- First, we calculate the latency as T_c in each stage.
 - $T_{c1} = 5 + .5 = 5.5$ ns
 - $T_{c2} = 4 + .5 = 4.5$ ns
 - System clock has to follow the slower T_c , hence, Circuit $T_c = 5.5$ ns
 - Therefore, throughput $1/T_c = 182$ MHz. However, latency L is now $5.5 \times 2 = 11$ ns (why?)



Throughput Calculation – 3 Stage Pipeline

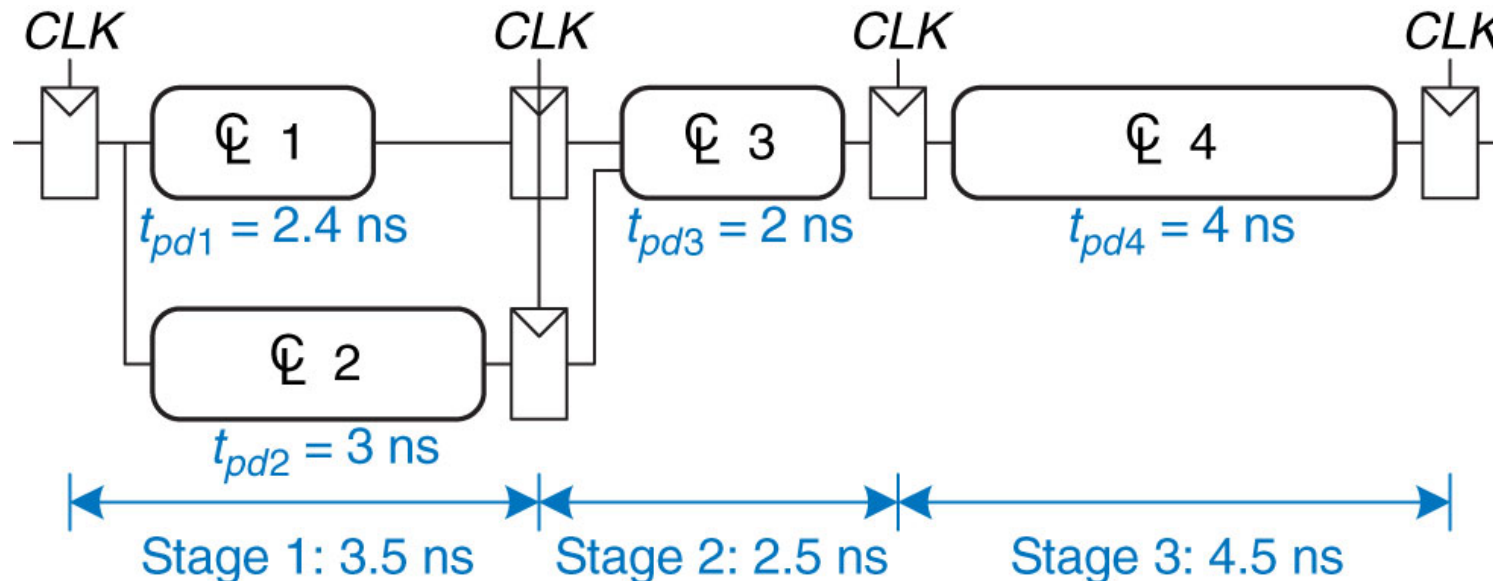- Again, we calculate the latency as T_c in each stage.
 - $T_{c1} = 3 + .5 = 3.5$ ns
 - $T_{c2} = 2 + .5 = 2.5$ ns
 - $T_{c3} = 4 + .5 = 4.5$ ns
 - Therefore, throughput $1/T_c = 1/4.5\text{ns} = 222$ MHz. However, latency $L = 13.5$ ns



Pipelining Limitation

- Pipelining is very powerful technique to increase the throughput. However, it assumes there are no dependencies between tokens (or tasks).
- In many cases, pipelining is of no significant use due to the dependencies between processes.
- Imagine in the cookie example if we had only one tray to use!!
- So in some situations, we experience the latency delay with no real throughput enhancement.

To Do List

- Review lecture notes
- Create an account on EDA Playground
- Study chapter 4