

3.10 inputs: CLK, J, K

outputs: Q

Hw 2


CLK	J	K	Q+
0	0	0	Q
0	0	1	Q
0	1	0	Q
0	1	1	Q
1	0	0	Q
1	0	1	0
1	1	0	1
1	1	1	\bar{Q}

0xx | Q

row reduction of

J	K	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q+ = J\bar{Q} + \bar{K}Q$$

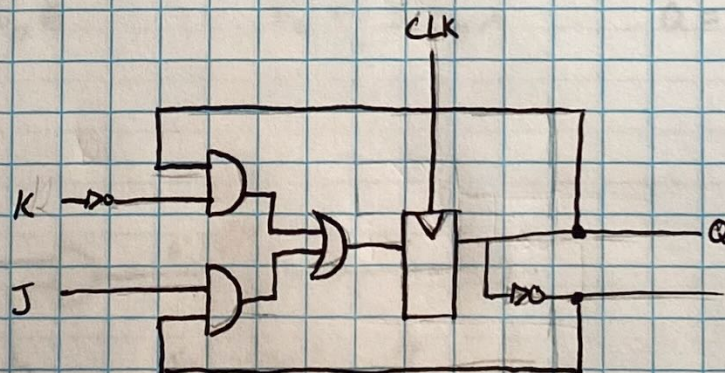

3.22 Each node in the finite state machine describes the circuit's state at an instance as a result of the previous state. ~~every~~
~~current state~~

Figure 3.69 identifies subset AB from the given binary input set. This assumes A or \bar{A} represents the zeroth and even positions while B or \bar{B} represents the odd positions.

S_1	S_0	Q	Current		Next	
			State	A B	State	Q
S_0	0	0	0	0	0 0	0
S_1	0	1	0	0	0 0	0
S_2	1	0	0	0	0 1	0
			0	1	0 0	0
			0	1	1 0	1
			1	0	0 0	0
				x x		

S_1	S_0	AB
00	00	
01	01	1 1
11	11	x x x x
10	10	


S_1	S_0	AB
00	00	1 1
01	01	
11	11	x x x x
10	10	

S_1	S_0	Q
0	0	
1	1	x

$$S'_1 = S_0 B$$

$$S'_0 = \bar{S}_1 \bar{S}_0 A$$

$$Q = S_1$$

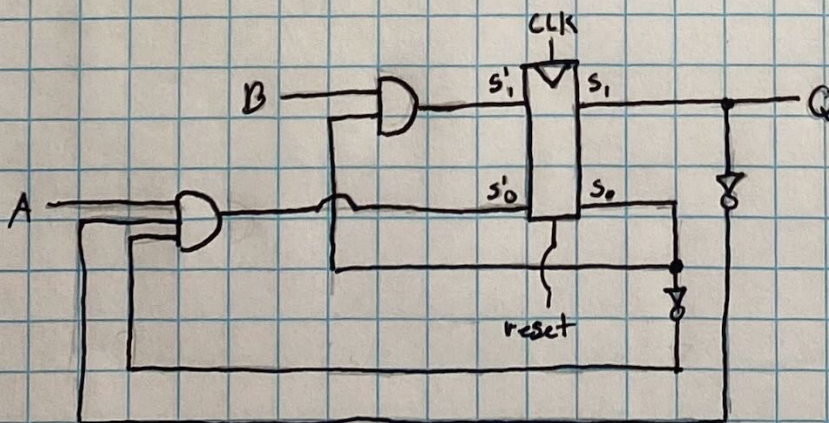

3.23 Similar to the previous state machine, figure 3.70 identifies successions of AB within the binary input set; however, it uses a mealy machine as opposed to a moore machine.

	S_1, S_0	Current State	A B	Next State	Q
S0	0 0	0 0	0 x	0 0	0
S1	0 1	0 0	1 x	0 1	0
S2	1 0	0 1	x 0	0 0	0
		0 1	x 1	1 0	0
		1 0	0 0	0 0	0
		1 0	0 1	0 0	0
		1 0	1 0	0 0	0
		1 0	1 1	1 0	1

$S_1, S_0 \backslash AB$	00	01	11	10
00				
01		1 1		
11				
10				1


$S_1, S_0 \backslash AB$	00	01	11	10
00			1 1	
01				
11				
10				

$S_1, S_0 \backslash AB$	00	01	11	10
00				
01				
11				
10				1

$$S'_1 = \bar{S}_1 S_0 B + S_1 \bar{S}_0 AB$$

$$S'_0 = \bar{S}_1 \bar{S}_0 A$$

$$Q = S_1 \bar{S}_0 AB$$

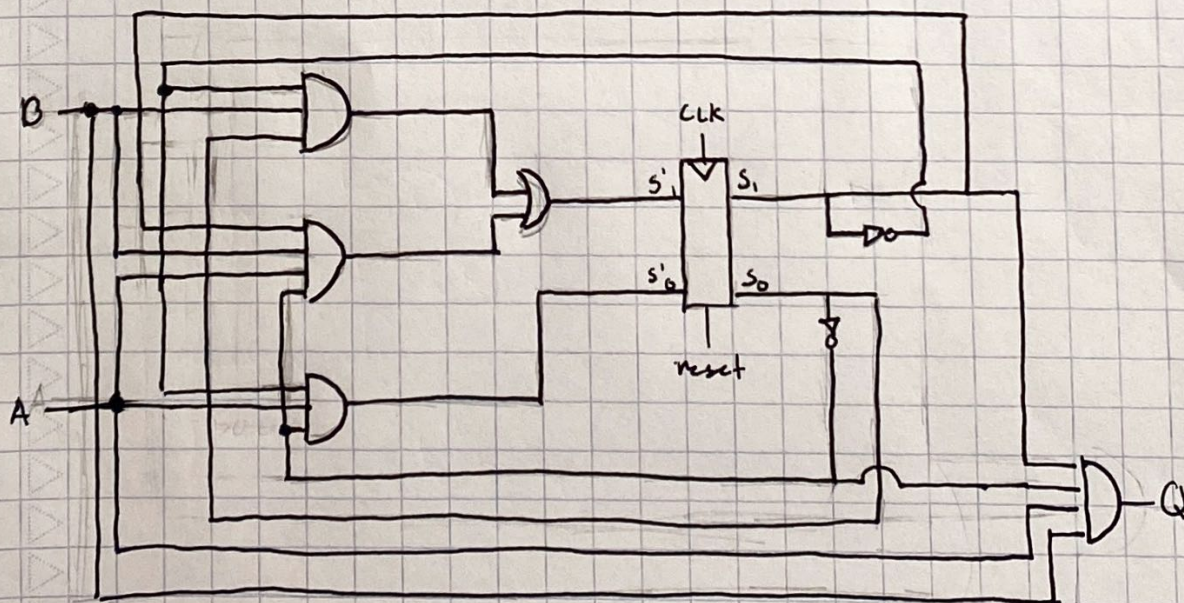

3.24

Current
State

A B

Next

State

0 0 0

0 x

0 0 1

0 0 0

1 x

0 0 0

0 0 1

x x

0 1 0

0 1 0

x x

0 1 1

0 1 1

x 0

1 0 0

0 1 1

x 1

0 1 1

1 0 0

x x


1 0 1

1 0 1

x x

0 0 0

	s_2	s_1	s_0	L_0	L_1	L_0
s0	0	0	0	0	0	1
s1	0	0	1	0	1	1
s2	0	1	0	1	0	1
s3	0	1	1	1	0	0
s4	1	0	0	1	0	0
s5	1	0	1	1	0	1

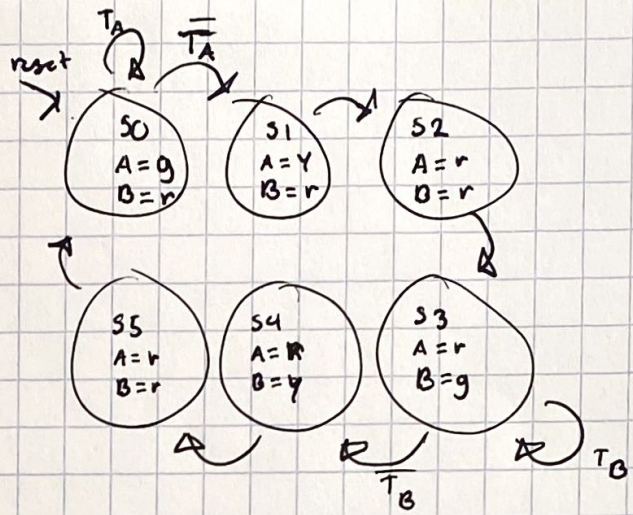

	L_1	L_0
g	0	0
y	0	1
r	1	0

3.27

current

Next

state

state

 $s_2 s_1 s_0$ $s'_2 s'_1 s'_0$

0 0 0

0 0 1

0 0 1

0 1 1

0 1 1

0 1 0

0 1 0

1 1 0

1 1 0

1 1 1

1 1 1


1 0 1

1 0 1

1 0 0

1 0 0

0 0 0

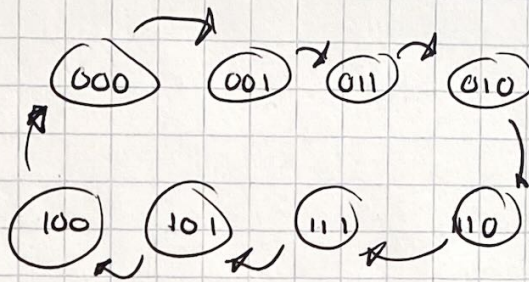

$s_2 \backslash s_1 s_0$	00	01	11	10
0				1
1		1	1	1


$$s'_2 = s_2 s_0 + s_1 \bar{s}_0$$

$s_2 \backslash s_1 s_0$	00	01	11	10
0		1	1	1
1				1

$$s'_1 = \bar{s}_2 s_0 + s_1 \bar{s}_0$$

$s_2 \backslash s_1 s_0$	00	01	11	10
0	1	1		
1			1	1

$$s'_0 = \bar{s}_2 \bar{s}_1 + s_2 s_1$$

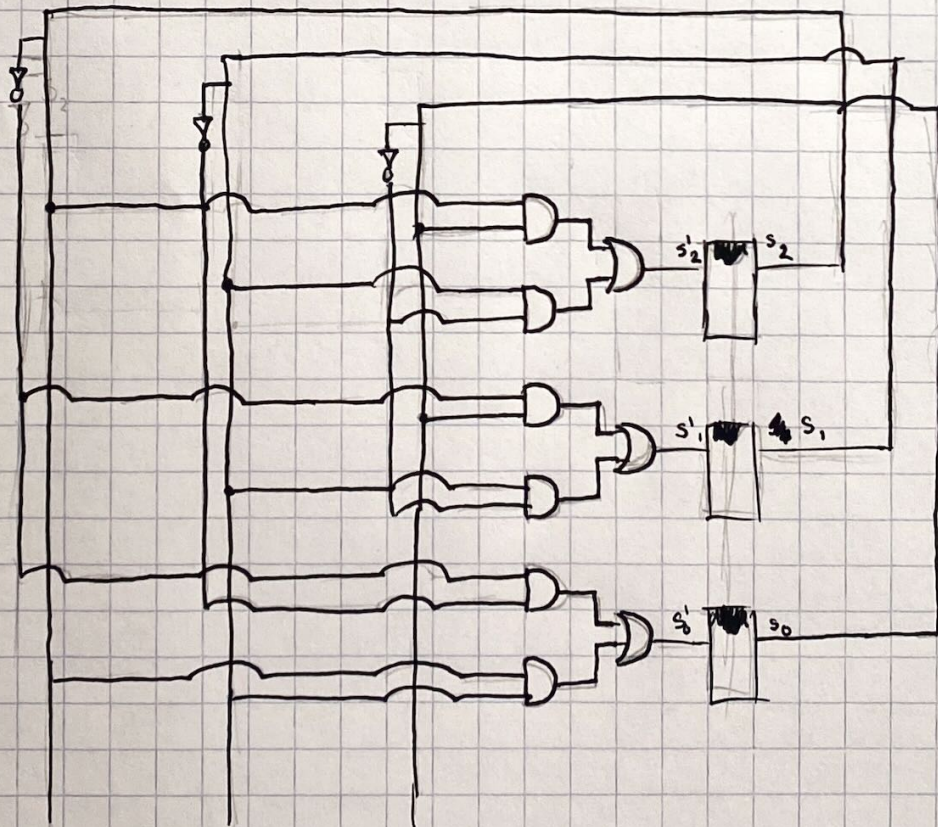


3.31 $Q = s_1 + s_0$
 $s'_1 = x \bar{s}_1$
 $s'_0 = s_1 + \bar{s}_0$

* because Q depends only on states, it
 is a moore machine


s_1, s_0	x	s'_1, s'_0	Q
0 0	0	0 1	0
0 0	1	0 1	0
0 1	0	0 0	1
0 1	1	1 0	1
1 0	0	0 1	1
1 0	1	0 1	1
1 1	0	0 1	1
1 1	1	0 1	1

s_1, s_0
s_0 0 0
s_1 0 1
s_2 1 0
s_3 1 1

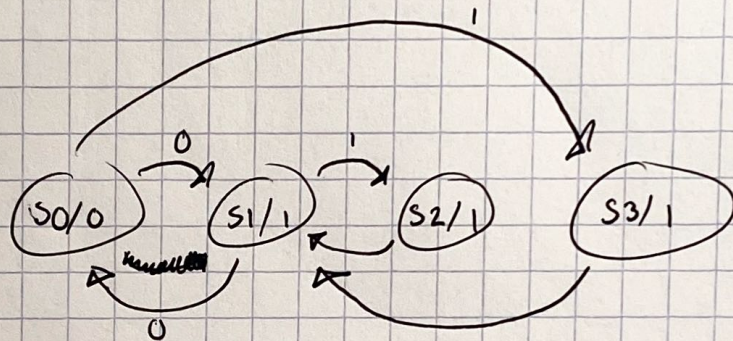given a binary input set,
 the state machine identifies
 substrings that contain a
 minimum of two elements
 in which the last element
 is not a 0.



3.33

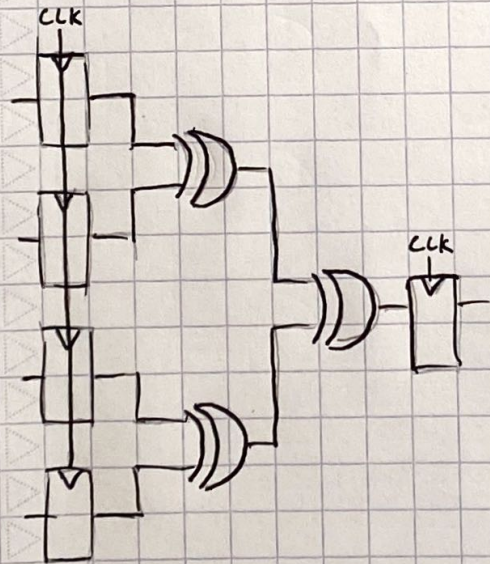

$$t_{\text{pd}} = 2 \times (100 \text{ ps}) = 200 \text{ ps}$$

$$t_{\text{cd}} = 2 \times (55 \text{ ps}) = 110 \text{ ps}$$

$$T_c \geq (70 + 200 + 60) = 330 \text{ ps}$$

$$f = 1/330 \text{ ps} = 3.03 \text{ GHz}$$

$$t_{\text{skew}} < [(50 + 110) - 20] = 140 \text{ ps}$$