

CS4341 Digital Logic & Computer Design

Lecture Notes 8

Omar Hamdy

Assistant Professor

Department of Computer Science

Review: Karnaugh Map (K-Map)

- A K-map is a diagram made of a collection of adjacent squares:
 - Each square represents a minterm
 - The collection of squares is a graphical representation of a Boolean function
 - Adjacent squares differ in the value of one variable only
 - Alternative algebraic expressions for the same function are derived by recognizing patterns of squares
- The K-map can be viewed as a reorganized version of the truth table

Review: Importance of K-Map

- K-Maps provide means of:
 - Finding optimum or near optimum
 - SOP and POS standard forms
 - Two-level AND/OR and OR/AND circuits
 - Visualizing concepts related to manipulating Boolean expressions
 - Demonstrating concepts used by computer-aided design programs to simplify large circuits

2-Variable K-Map

- If we represent each minterm as a box, then we have:


$$m_0 = x'y'$$

$$m_1 = x'y$$


$$m_2 = xy'$$

$$m_3 = xy$$

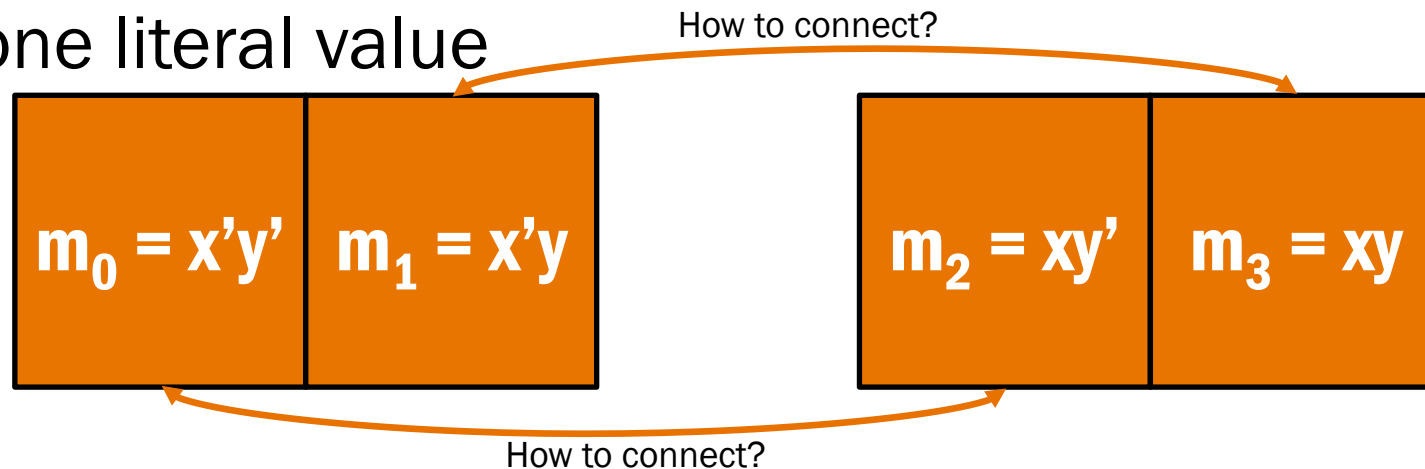
- We need to assemble the boxes such that adjacent boxes differ in exactly one literal value



2-Variable K-Map

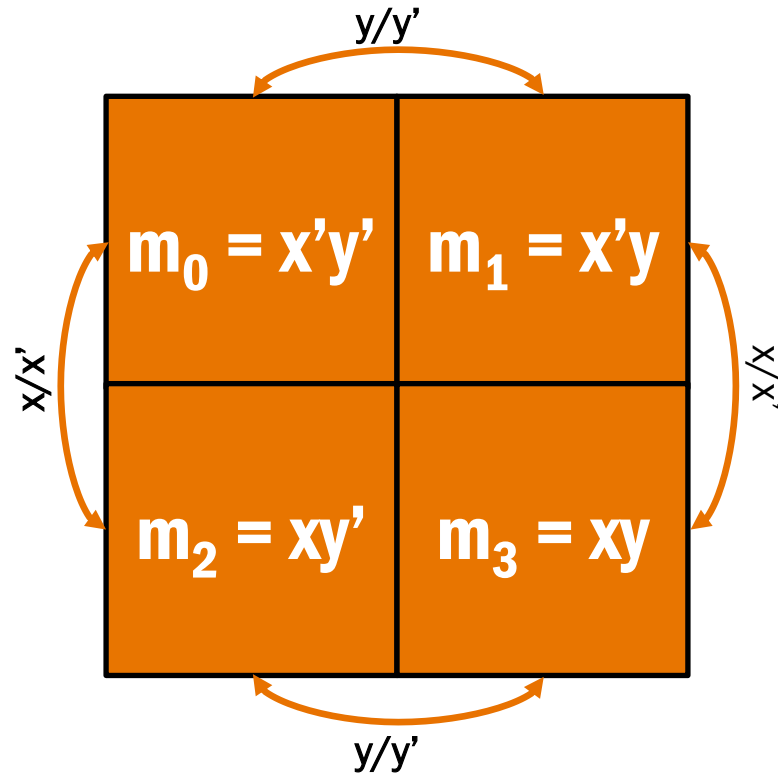

2-Variable K-Map

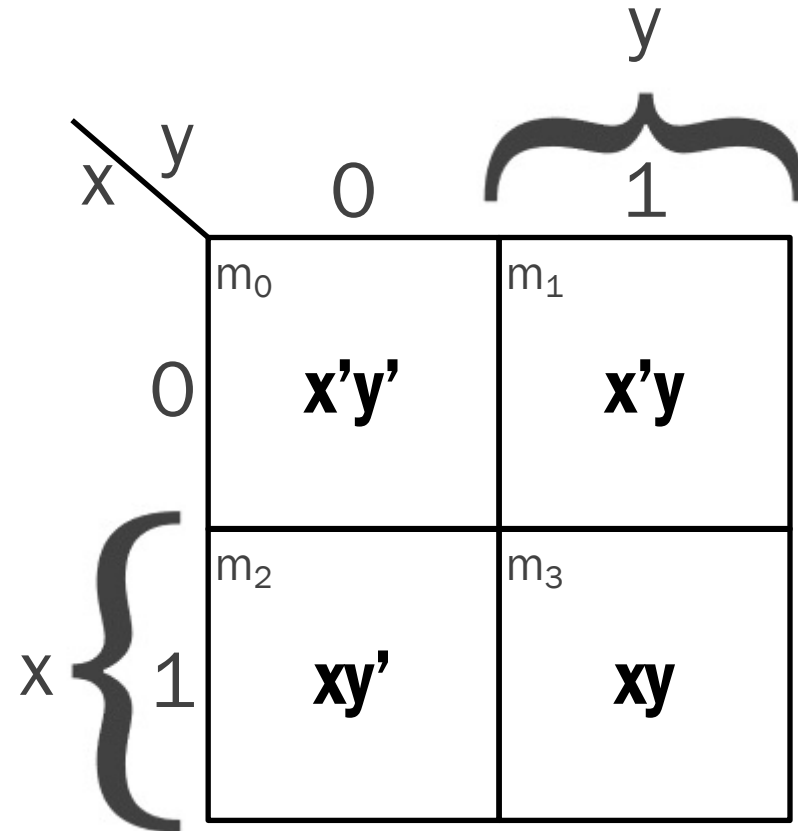

2-Variable K-Map Minimization

- Use K-Map to simplify the Boolean function expressed in the following truth table

Input Values (x,y)	Function Value $F(x,y)$
0 0	1
0 1	0
1 0	1
1 1	1

Step 1: represent the truth table in a K-Map diagram

$x \backslash y$	$y = 0$	$y = 1$
$x = 0$	1	0
$x = 1$	1	1

2-Variable K-Map Minimization

➤ Using algebraic simplification:

➤ $F(x,y) = m_0 + m_2 + m_3$

➤ $F = x'y' + xy' + xy$

➤ $F = (x' + x)y' + xy = (y' + x)(y' + y) = x + y'$

➤ Using K-Map simplification:

➤ Two adjacent 1s means one of the two variables is not impacting the output and can be ignored

$x \backslash y$	$y = 0$	$y = 1$
$x = 0$	1	0
$x = 1$	1	1


➤ $F =$ sum of all the simplified terms (prime implicants).

➤ $F = x + y'$

x variable can be ignored. The output = y'

y variable can be ignored. The output = x

3-Variable Adjacency View

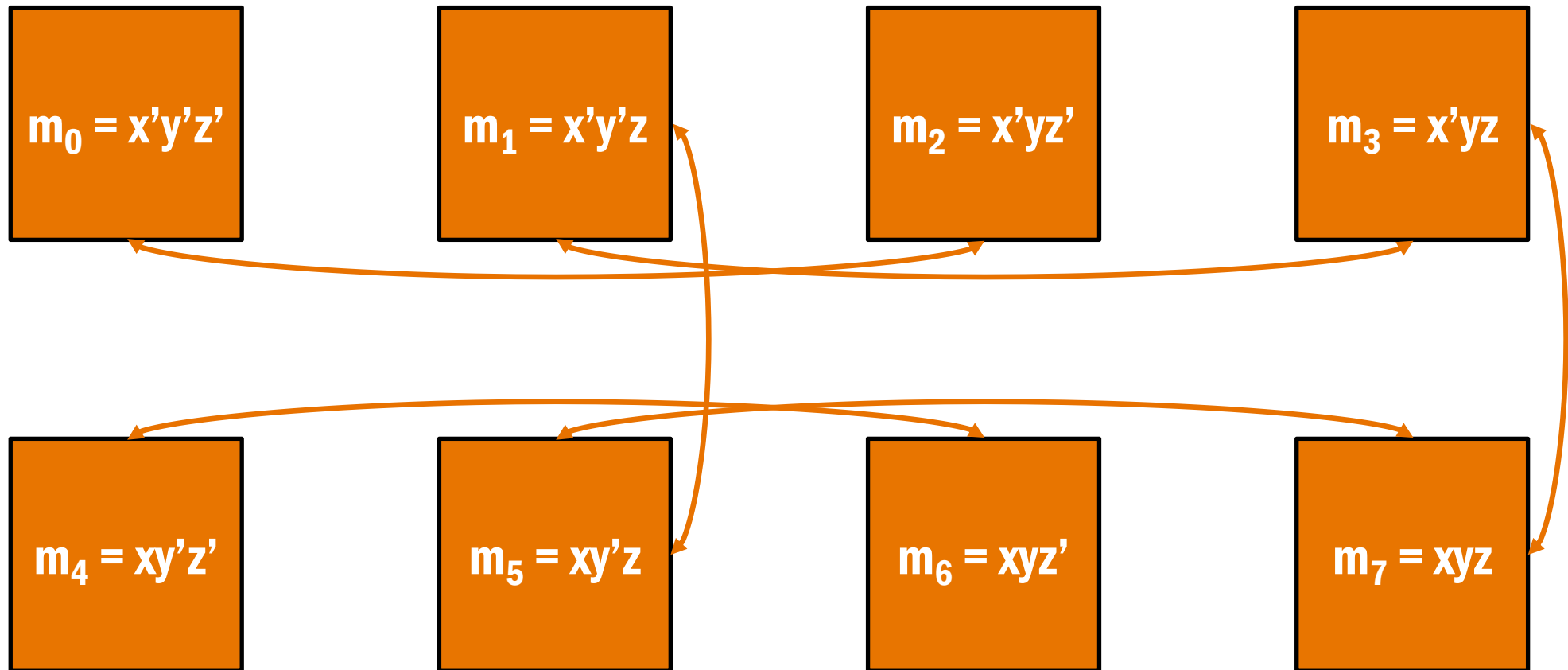

3-Variable K-Map

A 3-Variable K-Map diagram showing a 2x4 grid of cells. The columns are labeled with yz values: 00, 01, 11, and 10. The rows are labeled with x values: 0 and 1. Each cell contains a minterm label (m₀ to m₇) and a Boolean expression. Three groups are indicated by curly braces: a horizontal brace over the top row labeled 'y', a vertical brace on the left labeled 'x', and a horizontal brace under the bottom row labeled 'z'.

$x \backslash yz$	00	01	11	10
0	m_0 $x'y'z'$	m_1 $x'y'z$	m_3 $x'yz$	m_2 $x'yz'$
1	m_4 $xy'z'$	m_5 $xy'z$	m_7 xyz	m_6 xyz'

Combining Squares

- By finding largest possible 2^n squares and by combining squares, we reduce number of literals in a product term, hence reducing the gate cost
- On a 3-variable K-Map:
 - One square represents a minterm with 3 variables
 - Two adjacent squares represent a term with 2 variables
 - Four adjacent squares represent a term with 1 variable
 - Eight adjacent square is the function 1 (no variables)

Minimization Example

➤ Minimize (simplify) $F = \sum(2,3,6,7)$

x \ yz		00		01		11		10	
		m ₀		m ₁		m ₃		m ₂	
x	0	0	0	0	0	1	1	1	1
	1	0	0	0	0	1	1	1	1

➤ $F = \sum(2,3,6,7) = y$

➤ Using Boolean algebra:

➤ $F = x'yz' + x'yz + xyz' + xyz$

➤ $= x'yz + xyz + x'yz' + xyz'$

➤ $= yz + yz' = y$


Visual Simplification

- Now we understand how to construct and read a k-map, we can simplify its visual to make it less busy diagram

	0	1	3	2
			1	1
X	4	5	7	6
			1	1
			Z	

Minimization Example

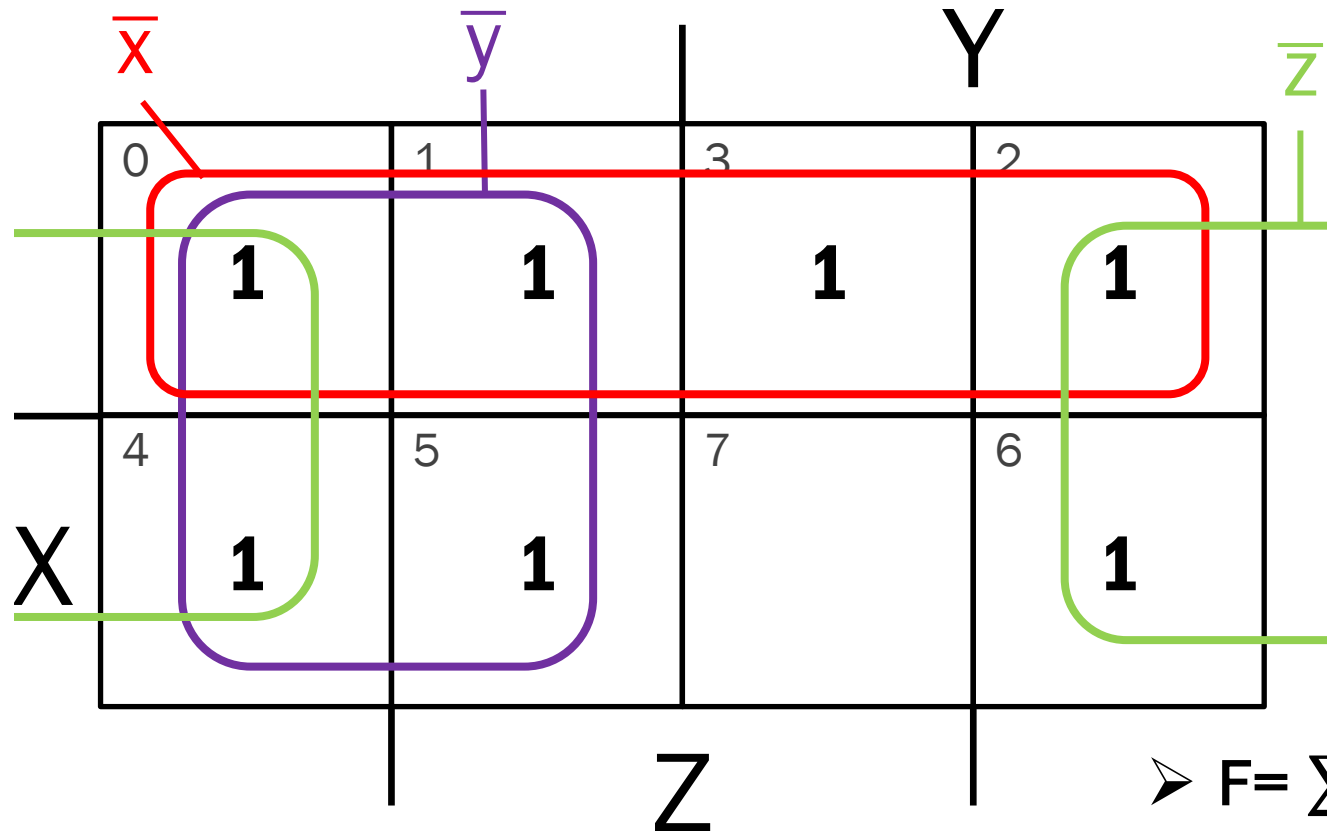➤ Describe $F(x, y, z)$ in its minimized form



➤ $F = \sum(0, 1, 2, 3, 4, 5, 6) = x' + y' + z'$

4-Variable K-Map

		\overline{Y}		Y		
		yz				
		00	01	11	10	
W	wx	0	1	3	2	
	00	$m_0 = \overline{w} \overline{x} \overline{y} \overline{z}$	$m_1 = \overline{w} \overline{x} \overline{y} z$	$m_3 = \overline{w} \overline{x} y z$	$m_2 = \overline{w} \overline{x} y \overline{z}$	\overline{X}
	01	$m_4 = \overline{w} x \overline{y} \overline{z}$	$m_5 = \overline{w} x \overline{y} z$	$m_7 = \overline{w} x y z$	$m_6 = \overline{w} x y \overline{z}$	
	11	$m_{12} = w x \overline{y} \overline{z}$	$m_{13} = w x \overline{y} z$	$m_{15} = w x y z$	$m_{14} = w x y \overline{z}$	X
	10	$m_8 = w \overline{x} \overline{y} \overline{z}$	$m_9 = w \overline{x} \overline{y} z$	$m_{11} = w \overline{x} y z$	$m_{10} = w \overline{x} y \overline{z}$	\overline{X}
		\overline{z}	z	\overline{z}		

To Do List

- Review lecture notes, and try the examples yourself
- Study chapter 2
- Work on assignment 1