

# CS4341 Digital Logic & Computer Design

## Lecture Notes 22

---

**Omar Hamdy**

Assistant Professor

Department of Computer Science

# Digital Building Blocks

- Now it is time to go one-level up in our abstraction hierarchy to introduce more complex digital components, how they can be used and interconnected, rather than the internal build of each.
- These building blocks are the basis for the microprocessor design
- The scope of our study includes:
  - Arithmetic circuits: addition, subtraction, comparators, ALUs, shifters/rotators, multiplication and division
  - Sequential building blocks: counters and shift registers
  - Memory arrays: memory cells, DRAM, SRAM and ROM
  - Logic arrays: programmable logic arrays (PLAs) and Field Programmable Gate Array (FPGA)

# Binary Addition


*Start with the least significant bit (rightmost bit):*

- Add each pair of bits
- Include the carry in the addition, if present
- Discard the carry if it exceeds the available maximum number size (overflow)

carry		1	1	1	1			
	0	0	1	1	0	1	1	0
								(54)
+	0	0	0	1	1	1	0	1
								(29)
<hr/>								
	0	1	0	1	0	0	1	1
								(83)
bit position:	7	6	5	4	3	2	1	0
 
# Binary Addition Circuits: Half Adder


- 1-bit half adder is the simplest addition building block. It has two 1-bit inputs A & B and two 1-bit outputs S and  $C_{out}$ .
- S is the sum of A & B, and if the addition is  $> 1$ , then  $C_{out}$  and S together represent the result of the addition (2).
- Careful study of the truth table shows that S is the A XOR B, and  $C_{out}$  is AB
- The half adder cannot be used for more than 1-bit numbers addition (why?)



$$S = A \oplus B$$
$$C_{out} = AB$$
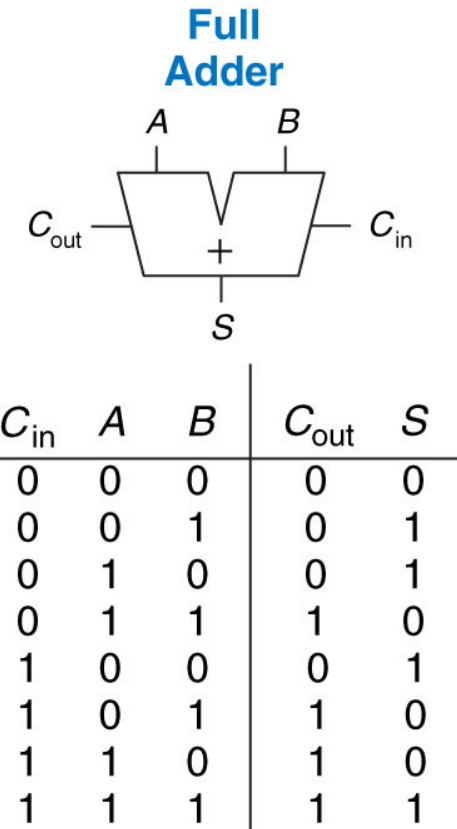
# Binary Addition Circuits: Full Adder


- A full adder introduces a 3<sup>rd</sup> input  $C_{in}$  to the half adder circuit
- This allows the circuit to accept carry from a previous bit-addition.
- Careful study of the truth table can verify the functional logic of  $S$  and  $C_{out}$
- Recall XOR of  $N$  inputs produces a 1 if the input has odd number of 1, and 0 otherwise.
- $S = A \oplus B \oplus C$
- $C_{out} = AB + (A + B) C_{in}$



$$S = A \oplus B \oplus C_{in}$$


$$C_{out} = AB + AC_{in} + BC_{in}$$

# Full Adders Circuit Implementation

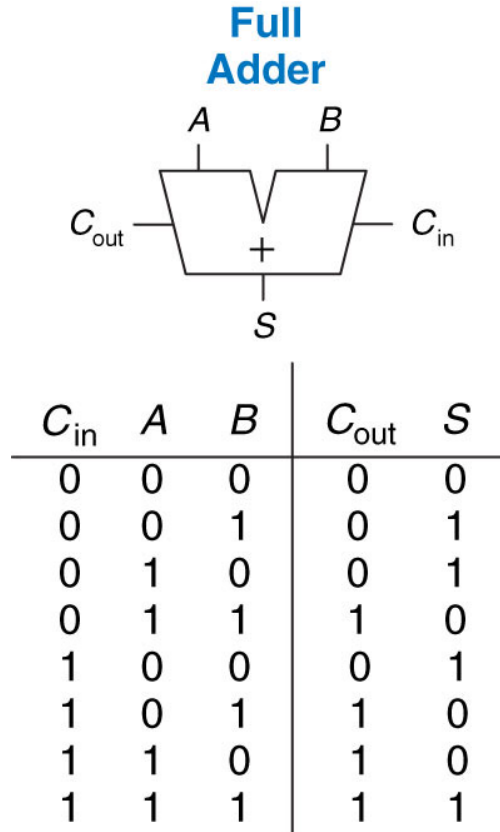


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

 

The full adder can be simplified further by noticing that  $C_{out}$  can be expressed as  $AB + C_{in}(A \oplus B)$  (why?)


# Full Adders - Simplified

 

$C_{in}$	$A$	$B$	$C_{out}$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + C_{in}(A \oplus B)$$

 
 
# Carry Propagate Adder (CPA)


- Now we introduce an adder capable of adding more than one bit.
- The circuit is similar to the full adder, except that the inputs are two busses instead of single-bit each.
- The shown circuit is an abstraction, which requires implementation strategy
- Three common implementations are ripple-carry adder, carry-lookahead adder and prefix adder.




 
# CPA Implementation: Ripple-Carry

- The ripple carry is the simplest CPA implementation.
- To add two N-bit numbers, N full-adders are chained together: the  $C_{out}$  of one adder becomes the  $C_{in}$  of the next adder.
- That model is slow  $O(N)$ , and for large N, CPA can be very slow.
- $t_{ripple} = Nt_{FA}$



# CPA Implementation: Carry-Lookahead

- The ripple carry delay is caused by the fact that each full adders needs to wait for the carry from the previous full adders to be generated.
- To overcome this bad delay, we need to find a way to produce (compute) all the carries simultaneously and not in sequence.
- This will require added logic, and hence there needs to be a balance between the delay and the added circuit complexity.
- The basic idea is to design each adder circuit in a way that it only considers the inputs and ignores any interim outputs (intermediate carries).
- That means only consider A&B inputs and the initial  $C_{in}$  to the circuit.



# Carry-Lookahead Model

- Carry-lookahead uses a mathematical model to produce  $C_{in}$  simultaneously
- The model defines two terms Generate (G) and Propagate (P) as follows:
  - Generate is when  $C_{in}$  is 0, and the adder is generating a  $C_{out}$  of 1
    - From the truth table,  $G = AB$
  - Propagate is when  $C_{in}$  is 1, and the adder is propagating it to  $C_{out}$ 
    - From the truth table,  $P = A + B$ , and following same circuit simplification, we can say  $P = A \oplus B$
- Therefore,  $C_{out} = AB + (A \oplus B)C_{in} = G + PC_{in}$


$C_{in}$	$A$	$B$	$C_{out}$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1
  
# Calculating Carry-Lookahead

- First, we modify the full-adder circuit to produce G and P instead of  $C_{out}$ .
- For any full adder i:  $G_i = A_i B_i$  and  $P_i = A_i \oplus B_i$
- Therefore,  $C_{out(i)} = G_i + P_i C_{in(i)}$
- It then follows that  $C_{in(i+1)} = C_{out(i)}$
- For convenience, we will refer to  $C_{in(i+1)}$  as  $C_{i+1}$
- Therefore,  $C_{i+1} = g_i + p_i C_i$ 
  - $C_1 = g_0 + p_0 C_0$ , and  $C_2 = g_1 + p_1 C_1$
  - Then,  $C_2 = g_1 + p_1(g_0 + p_0 C_0) = g_1 + p_1 g_0 + p_1 p_0 C_0$
  - Then,  $C_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 C_0$
  - Also,  $C_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0$



# 3-Bit Carry Lookahead Circuit

 


$$C_3 = g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0C_0$$

$$C_2 = g_1 + p_1g_0 + p_1p_0C_0$$

$$C_1 = g_0 + p_0C_0$$
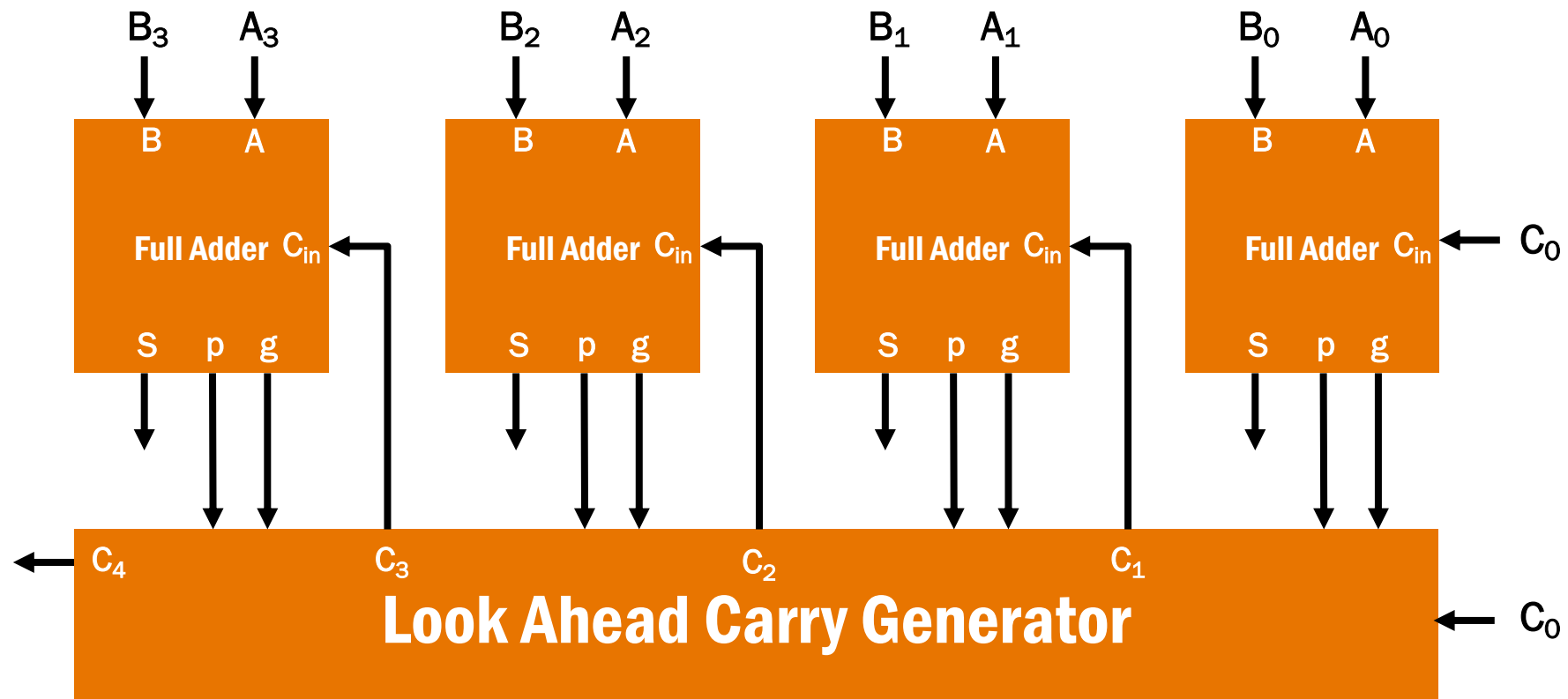
# CPA Implementation: Carry-Lookahead

- Putting the circuit all together, we get the following abstracted view



## Carry-Lookahead Limitations


- Recall  $C_4 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0C_0$
- Therefore, for the case of 4-bit carry lookahead adder, the final carry out  $C_4$  requires a 5-input OR gate, and 5, 4, 3 and 2-input AND gates.
- Therefore a 32-bit CLA will require 33-input gates, which is not practically feasible.
- Alternatively, 4-bit CLA's can be combined in a hierarchal manner.
- For example a 16-bit CLA can be implemented using four 4-bit CLAs and an additional level of carry lookahead logic.
- This will add delay to the overall circuit.

# Group Carry and Propagate

➤ The hierarchical model will require 4-bit CLA building block as follows

➤  $p_g = p_3 p_2 p_1 p_0$  follows

 
➤  $g_g = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 p_0 g_0$





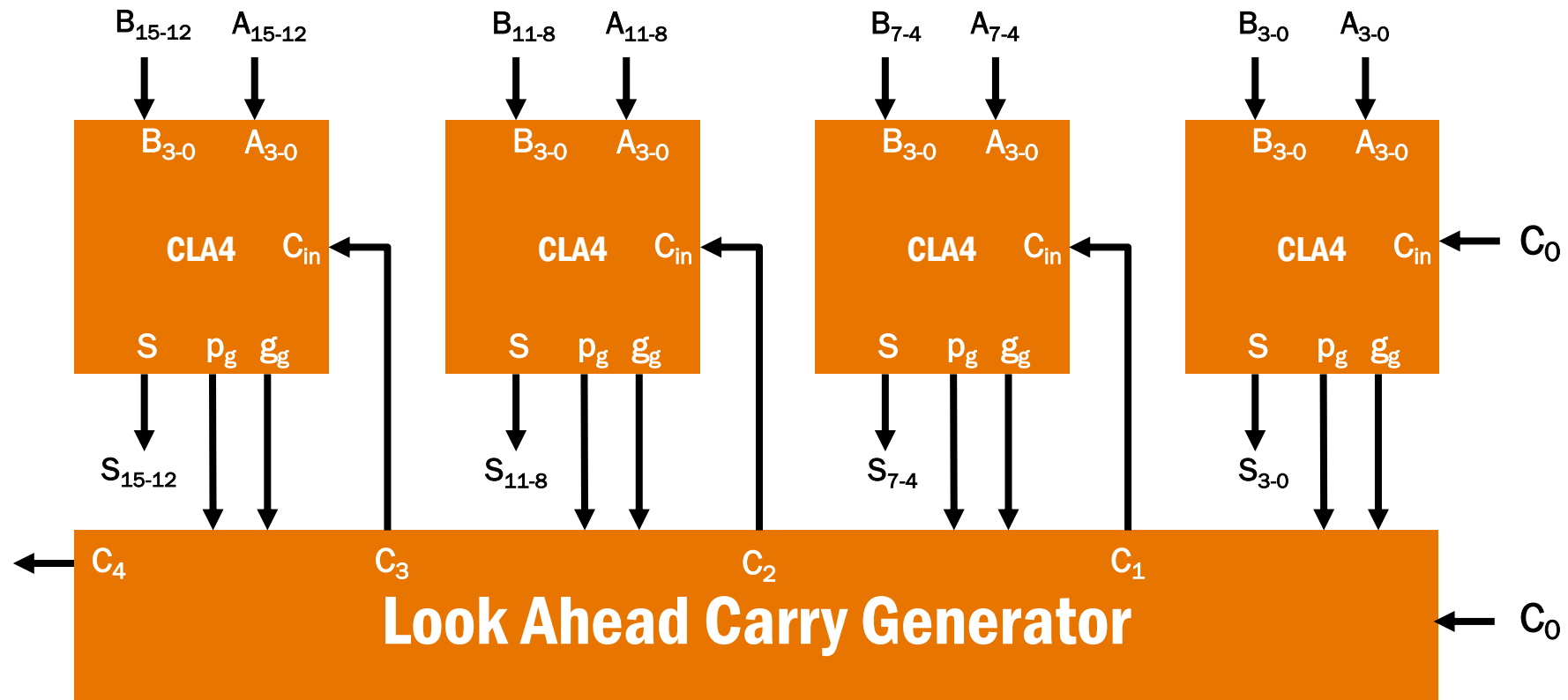
# CPA Implementation: Carry-Lookahead

- Putting the circuit all together, we get the following abstracted view




 
# Subtraction

- Subtraction can be done by adding A to the 2's complement of B.



  
# Comparators

- Comparator determines if two binary numbers are equal, or one is greater (smaller) than the other.
- Two common types:
  - Equality comparator: produces a 1 if A is equal to B (How?)
  - Magnitude comparator: produces a 1 if  $A < B$ , and 0 if  $A \geq B$  (How?)


 
# ALU



- Arithmetic/Logical Unit (ALU) combines a variety of mathematical and logical operations into a single unit.
- Therefore, the ALU needs an additional input  $F$  which tells the ALU which function to perform.
- A good ALU design efficiently uses the digital building blocks with minimum redundancy.
- Can you think of a design?



$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND $\bar{B}$
101	A OR $\bar{B}$
110	A - B
111	SLT

# ALU Internal Design

$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND $\bar{B}$
101	A OR $\bar{B}$
110	A - B
111	SLT

 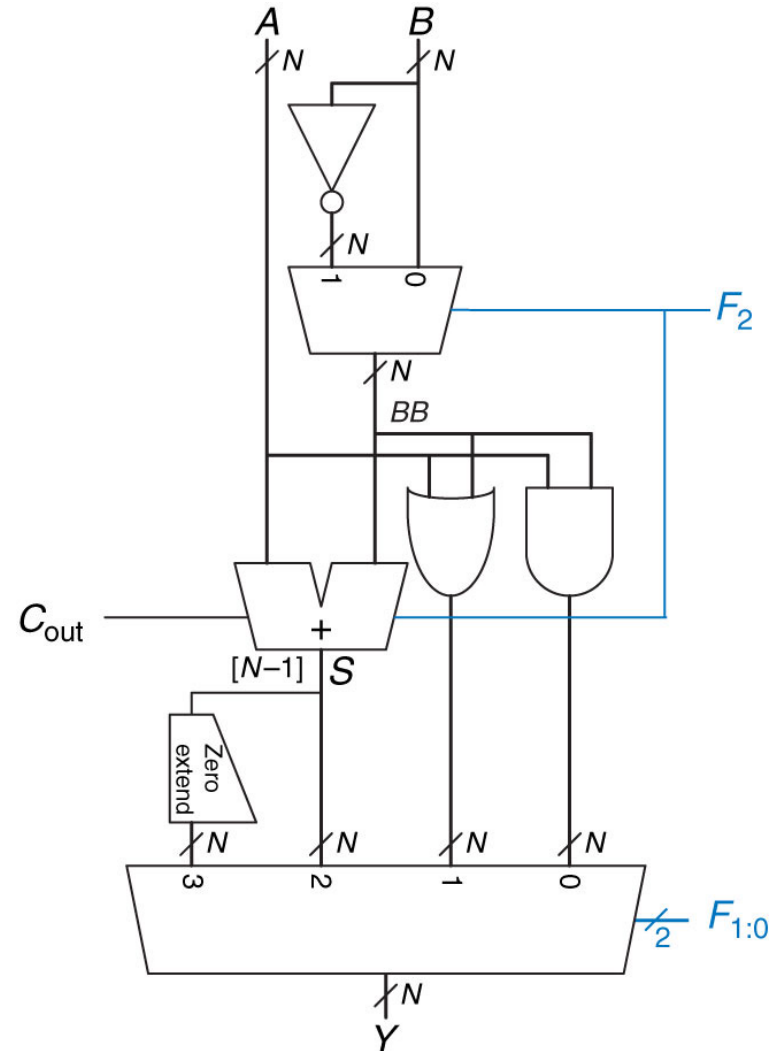

## To Do List

- Review lecture notes
- Study Chapter 5, sections 1 through 3