

CS4341 Digital Logic & Computer Design

Lecture Notes 12


Omar Hamdy

Assistant Professor

Department of Computer Science

Sequential Circuits

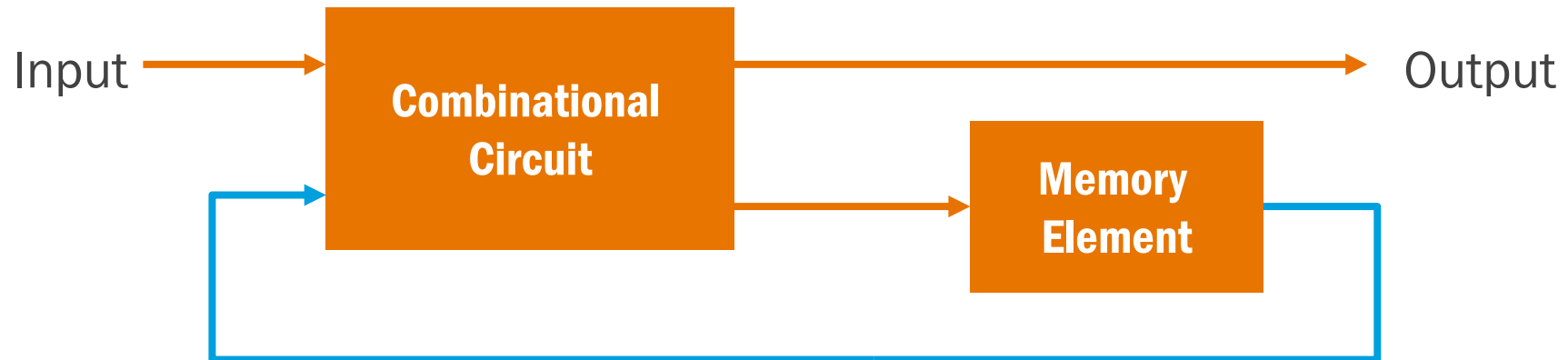- Sequential circuits are digital circuits that the output depends on:
 - current input (combinational circuit), and
 - system state: a memory device to preserve the output value



Example

- What is the key difference between these two locks?



Combinational: output depends only on input




Sequential: output depends on new and previous inputs

Sequential Circuit Types


- **Sequential circuits are differentiated by times at which:**
 - storage elements observe their inputs, and
 - storage elements change their state
- **Synchronous sequential circuits:**
 - Behavior is defined from knowledge of inputs at discrete instances of time
 - Storage elements observe inputs and can change state only in relation to a timing signal (clock pulses from a clock)
- **Asynchronous sequential circuits:**
 - Behavior is defined from knowledge of inputs at any instant of time
 - Storage elements observe inputs and can change state at any instant of time

Bistable Memory Building Block

 
- Bistable is a digital element with two stable states 0 and 1. If the output is 0, it stays 0 (stable), and if output is 1, it stays 1 (stable)



 - To analyze this cyclic element, we consider the status when Q is 0 and when Q is 1:



(a)

 


(b)

Bistable Memory Building Block

- An Element with N stable states conveys $\log_2 N$ of information
- The bistable state element has two stable states, hence it “stores” one bit of information (Q)
- Q holds a value from the past, which can be used to determine the future state of the circuit.
- The basic bistable elements are limited in their use, because we cannot control or change its status.
- More useful bistable elements should contain control inputs

SR Latches

 - SR latches are the basic asynchronous memory devices
- SR latches have two control inputs, S (set) and R (reset)




- SR latches have two famous implementations using NOR and NAND gates

SR Latch Behavior Study

- Study of the circuit behavior requires studying the input values as well as the present output values (Current State CS) to find the next output values (Next State NS)


S	R	Q	Q ⁺	Status
0	0	0	0	Memory
0	0	1	1	Memory
0	1	0	0	Reset
0	1	1	0	Reset
1	0	0	1	Set
1	0	1	1	Set
1	1	0	?	Forbidden
1	1	1	?	Forbidden

 

SR Latch Behavior Study

- Using the combining row technique, we can eliminate Q (right-most variable) from the truth table, and express the output Q^+ as 0, 1 or Q


S	R	Q^+	Status
0	0	Q	Memory
0	1	0	Reset
1	0	1	Set
1	1	?	Forbidden

 

- Algebraically: $Q^+ = S + R'Q$ (WHY? – Home Exercise)
- Home exercise: build the SR latch using NAND gates

SR Latch Memory Element

 
- SR latch is a bistable element with one bit of state stored in Q . However, the state can be controlled through the S and R inputs. When R is asserted, the state is reset to 0. When S is asserted, the state is set to 1. When neither is asserted, the state retains its old value



D Latch

- SR latches have multiple design concerns:
 - The undesired state with S & R are both 1.
 - The inputs are also responsible for the timing when the change should happen, and to preserve the status. Ideally, they should only be responsible for the status change.
- D Latches solve these two problems SR Latches have:
 - Instead of S/R, only one input and its inverted value are used
 - Another input *CLK* is responsible for when the element should consider the change.



D Latch

 

- When $CLK = 1$, the latch is *transparent*, and the data at D flows to Q.
- When $CLK = 0$, the latch is *opaque*, and blocks the data at D to flow to Q. Hence, the D latch retains its current state.
- Algebraically: $Q^+ = D$

D Latch Timing Problem

 
 
- Consider the following D Latch circuit, how will the circuit behave during an active *Clk* cycle? (Assume Y is initially 0)




Undesirable behavior

D Flip-Flop

 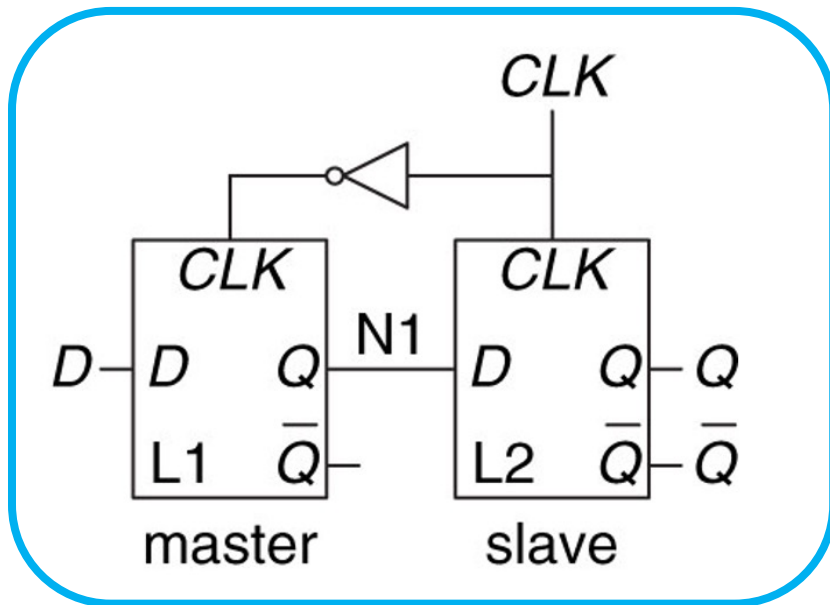- The solution of the D-Latch undesired behavior is to break the closed path from Y to itself.
- This is done using D flip-flop, which is built from two back-to-back D latches controlled by complementary clocks




D Flip-Flop

 

Condensed
Symbol

D Flip-Flop Analysis

 

- When CLK is 0, the master latch is transparent, and the slave is opaque. Hence, D value is propagated to $N1$
- When CLK is 1, the slave latch is transparent, and the master is opaque. Hence, $N1$ value is propagated to Q .
- From timing perspective: Whatever value was at N immediately before the CLK “rises” is copied to Q immediately after the CLK “rises”.
- Therefore, **a D flip-flop, copies D to Q on the *rising edge* of the CLK , and remembers (preserves) its state at all other times.**



To Do List

- Review lecture notes
- Study chapter 3 through 3.4.4