

CS4341 Digital Logic & Computer Design

Lecture Notes 4

Omar Hamdy

Assistant Professor


Department of Computer Science

Review: Truth Table

- *Truth table is a tabular listing of the values of a function for ALL possible combinations of values on its arguments*
- *Truth table is a useful tool to study the behavior of any Boolean function*


Review: Basic Logic Gates and Truth Table

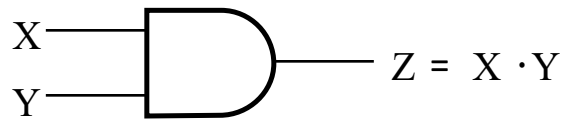➤ *Logic gates are simple digital circuit that implements the logical operators*




AND gate

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

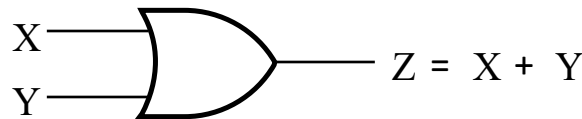

OR gate

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

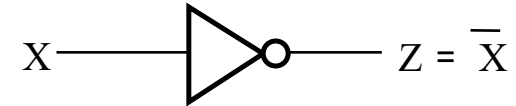

NOT gate or inverter









X	Z
0	1
1	0

Review: Example

➤ Evaluate the following logic function: $F(X, Y, Z) = X Y + \bar{Y} Z$


X	Y	Z	XY	\bar{Y}	$Z\bar{Y}$	$XY + Z\bar{Y}$
0	0	0	0	1	0	0
0	0	1	0	1	1	1
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	0	1	0	0
1	0	1	0	1	1	1
1	1	0	1	0	0	1
1	1	1	1	0	0	1

Waveform Behavior View

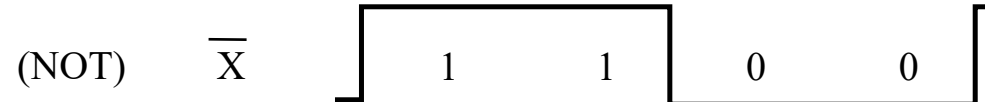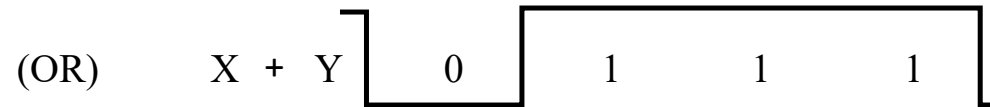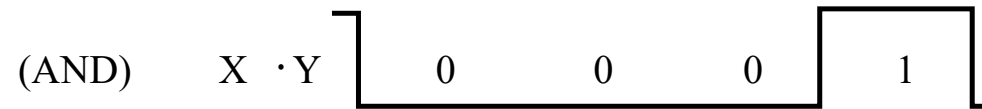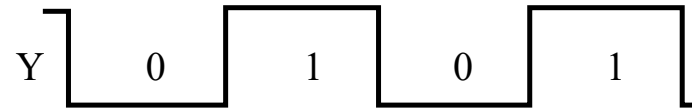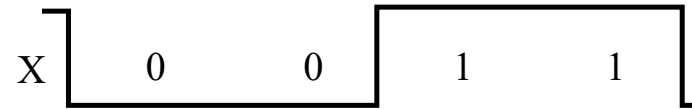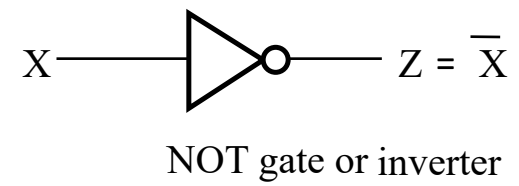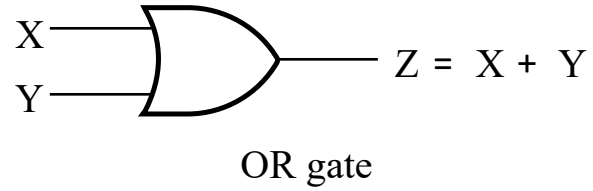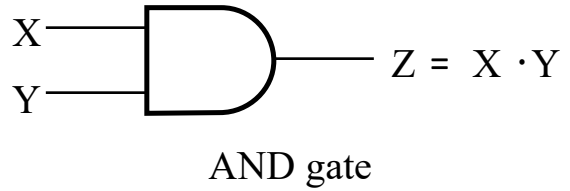


Logic Function Example

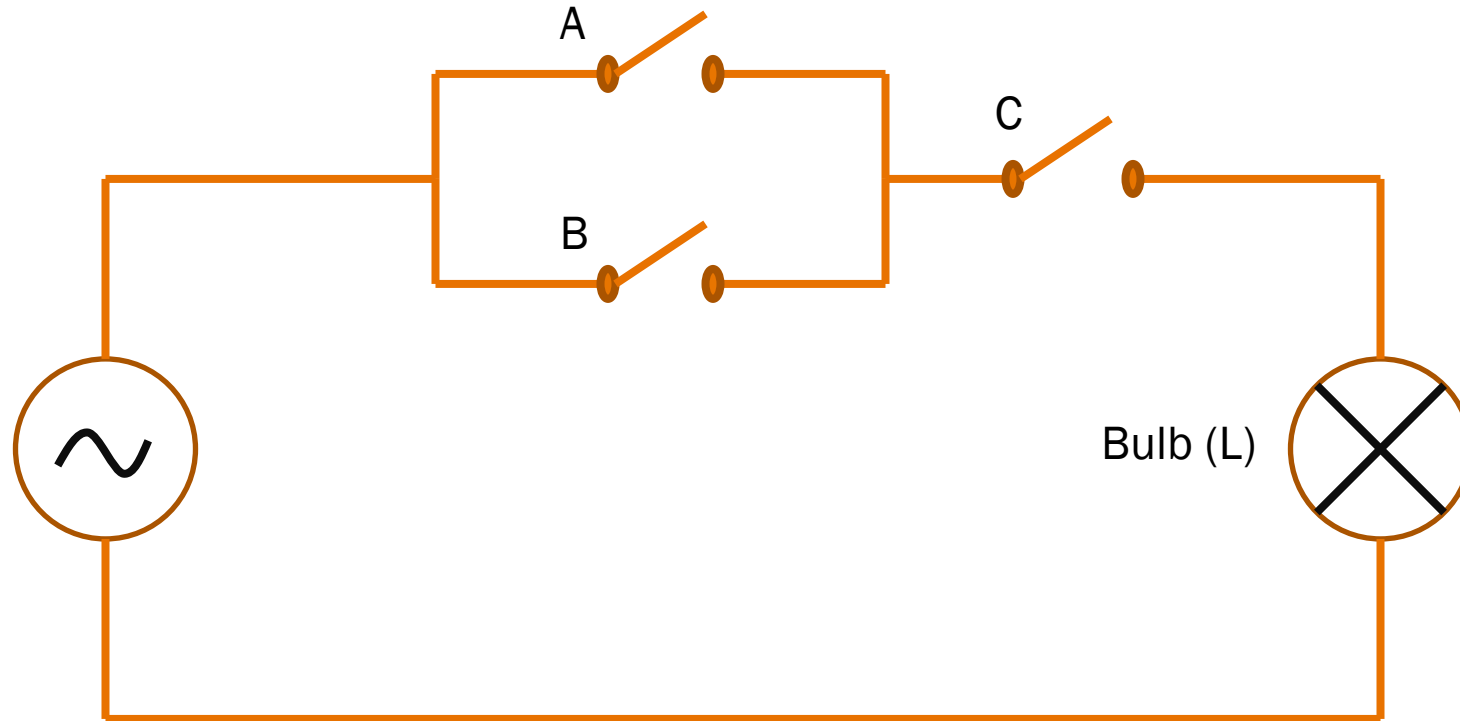➤ *Analyze the operation of the following circuit using the truth table. Write the logic function relating L to A , B , and C*



Solution Using Truth Table

A	B	C	L
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

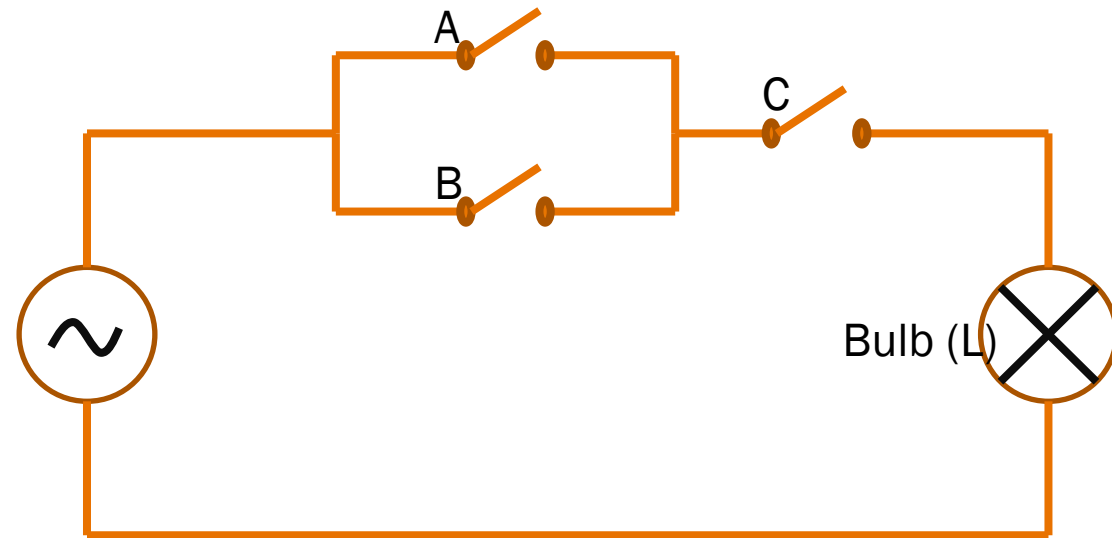


Solution Using Algebraic Function

- The Light is on if:
- A AND C are closed, OR
- B AND C are closed, OR
- A AND B AND C are closed

$$L = A.C + B.C + A.B.C$$

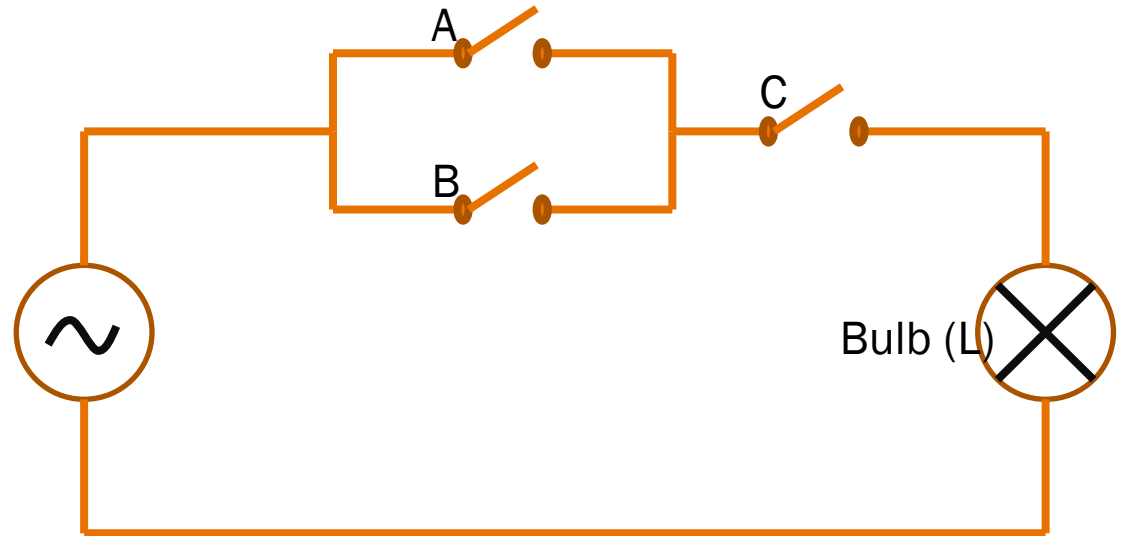Later we will see that $L = C.(A+B)$ (OPTIMIZED)









Combinational Circuits

- Logic functions are implemented using digital logic circuits.
- A digital circuit is composed of:
 - Items: An item is a circuit which implements some logical function
 - Nodes: A node is a connection (wire) that connects to external input, output or between inner items.
- There are two classes of digital logic circuits:
 - Combinational circuits: the output depends only on the current values of the input (memoryless)
 - Sequential circuits: the output depends on both current and previous input value (has memory)

Combinational Circuits

- Combinational circuits must meet three conditions:
 - Every circuit element is itself combinational.
 - Every node of the circuit is either designated as an input to the circuit or connects to exactly one output terminal of a circuit element
 - The circuit contains no cyclic paths: every path through the circuit visits each circuit node at most once.

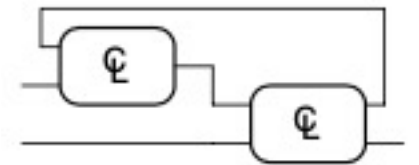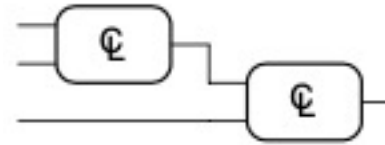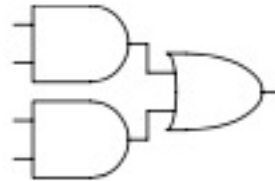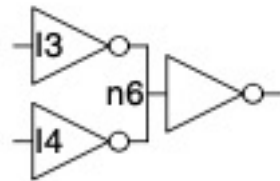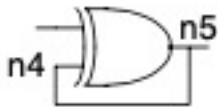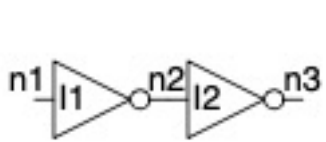Example: Determine the combinational circuits in the following



Boolean Algebra

➤ *In Binary Boolean Algebra:*

- We have a set of elements 0 and 1
- We have a set of operators that operate on those elements such as AND (\cdot), OR ($+$), and negation ($'$).
- We have $1' = 0$ and $0' = 1$
- Logic value TRUE has value 1
- Logic value FALSE has value 0

Operator Precedence

- Parenthesis ()
- NOT (Negation)
- AND
- OR
- Example: Show the order of execution of $\text{NOT } X + Y \cdot Z$
 - Answer: $X' + (Y \cdot Z)$

Boolean Expression

- Boolean expressions are formed by applying the operators to Boolean variables
- Boolean expressions (functions) could be represented by:
 - Equations
 - Logic gate diagram
 - Truth table

Duality of Boolean Expressions

- The dual of an algebraic expression is obtained by interchanging $+$ and \cdot and interchanging 0's and 1's.
- Example: Assume: $F = (A + B) \cdot C$, find $Dual(F)$
 - $Dual(F) = A \cdot B + C$
- Dual of a function generates a totally new function
- Dual of a function is **not** equal to the function
- Dual of a function is **not** equal to its complement

Duality Importance

- Every Boolean expression that is proven as true has a dual expression that is also true.
- Examples:

<i>Expression</i>	<i>Duality</i>
$x + 0 = x$	$x \cdot 1 = x$
$x + x = x$	$x \cdot x = x$

Postulates of Boolean Algebra

	Expression	Duality	Postulate
1	$X + 0 = X$	2 $X \cdot 1 = X$	Identity Element
3	$X + 1 = 1$	4 $X \cdot 0 = 0$	Domination
5	$X + X = X$	6 $X \cdot X = X$	Idempotence
7	$X + X' = 1$	8 $X \cdot X' = 0$	Complement
9	$X'' = X$		Involution
10	$X + Y = Y + X$	11 $X \cdot Y = Y \cdot X$	Commutative
12	$(X + Y) + Z = X + (Y + Z)$	13 $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	Associative
14	$X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$	15 $X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$	Distributive
16	$(X + Y)' = X' \cdot Y'$	17 $(X \cdot Y)' = X' + Y'$	DeMorgan's

Additional Rules

	Expression	Duality	Postulate
1	$X + (X \cdot Y) = X$	2 $X \cdot (X + Y) = X$	Absorption
3	$X + (X' \cdot Y) = X + Y$	4 $X \cdot (X' + Y) = X \cdot Y$	
5	$(X + Y) \cdot (X + Y') = X$	6 $(X \cdot Y) + (X \cdot Y') = X$	Logical Adjacency

Algebraic Manipulation

➤ Example: $F = AB + AC + AB' + AC'$

➤ $= AB + AB' + AC + AC'$

➤ $= A(B + B') + A(C + C')$

➤ $= A + A$

➤ $= A$

➤ Example: $F = x(x' + y)$

➤ $= xx' + xy$

➤ $= 0 + xy$

➤ $= xy$

Function Complement

- Complement of F is F'
- Complement of a function is obtained by interchange of 0's for 1's and 1's for 0's in the values of F in the truth table.
- We can also use DeMorgan's theorem to get F' .
- The following identities are very useful:
 - $(A + B)' = A' B'$ $A' + B' = (AB)'$
 - $(A+B+C)' = A' B' C'$ $A' + B' + C' = (ABC)'$

Function Complement Example

➤ Find the complement of $F = AB + C$

➤ Answer:

➤ $F' = (AB + C)'$

➤ Applying DeMorgan's theorem:

➤ $= (A' + B') \cdot C'$

➤ $= A'C' + B'C'$

Function Complement From Dual

- We can find the complement of a function by finding its dual then complementing each literal
- Example: $F = x'yz' + x'y'z$
 - $F(dual) = (x' + y + z') \cdot (x' + y' + z)$
 - $F(complement) = F' = (x + y' + z)(x + y + z')$

To Do List

- Review lecture notes
- Study 2.1 to 2.3.3