

# CS4341 Digital Logic & Computer Design

## Lecture Notes 11

---

**Omar Hamdy**

Assistant Professor

Department of Computer Science


## Example: Design Using MUX

- Design the Boolean function  $F = AB' + B'C' + A'BC$  using 8x1 mux

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$Y = \overline{A}\overline{B} + \overline{B}\overline{C} + \overline{A}BC$$



(a)

 

(b)

 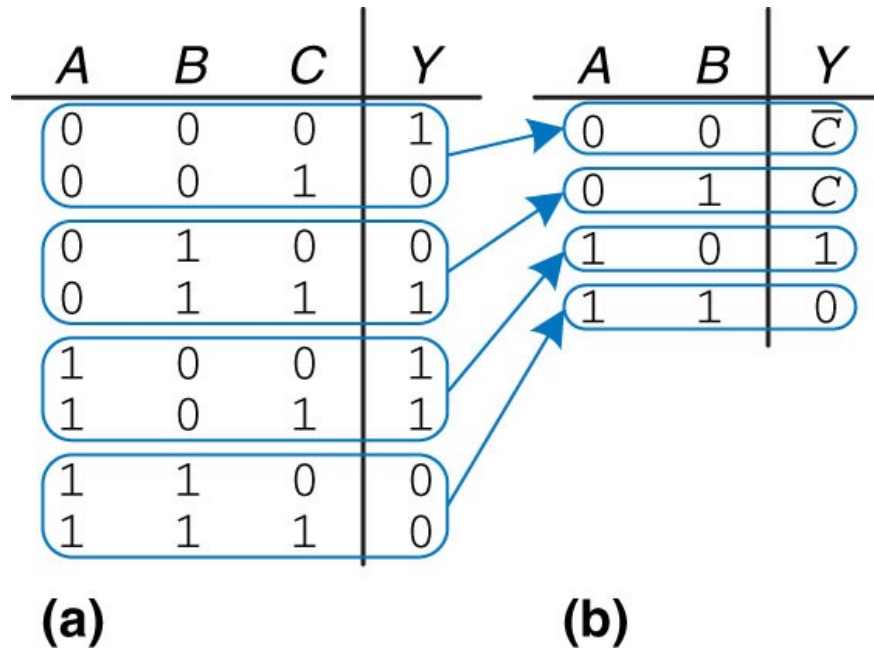
# Example: Design Using MUX

- Design the Boolean function  $F = AB' + B'C' + A'BC$  using 4x1 mux



 
# Decoders


- An  $n \times m$  decoder is a combinational circuit that converts binary information from  $n$  input lines to  $m$  output lines, where  $m \leq 2^n$
- Output values of decoders are mutually exclusive: exactly one output is 1 for any given input combination (**address**).



## 2:4 Decoder

 


$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

# Decoders with Active-High Enable $E$


EN	A <sub>1</sub>	A <sub>0</sub>	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

(a)

 


(b)

# Hierarchical Decoder Design

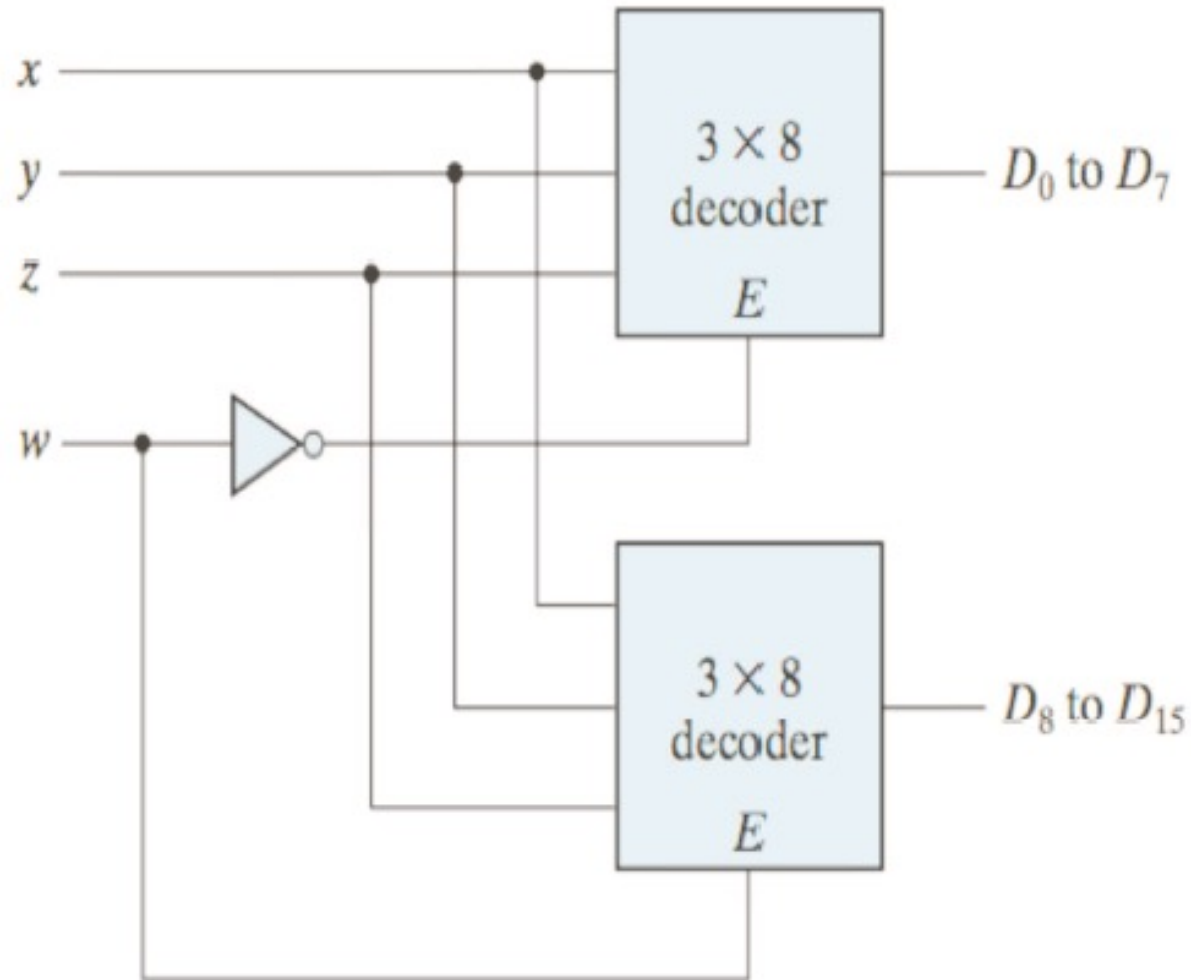
 
# Timing

- Until now, we assumed there is a 0-time for input values to propagate through the combinational circuit to produce the output.
- The reality is, time is one of the key design factors as output takes time to change as the input signals pass through the circuit.




- A timing diagram shows the transient response of the circuit when input changes.
- Transition from Low to High is called rising edge
- Transition from High to Low is called falling edge
- A 50% point is the point when a signal is half way between High and Low
- Delay is measured from the 50% point of the input signal to the 50% point of the output signal


 
# Propagation and Contamination Delay

- Combinational logic is characterized by its propagation delay and contamination delay.
- The propagation delay,  $t_{pd}$ , is the maximum time from when an input changes until the output or outputs reach their final value.
- The contamination delay,  $t_{cd}$ , is the minimum time from when an input changes until any output starts to change its value




# Delay Calculation

- At high-level, propagation and contamination delays are determined by the path a signal takes from input to output.
- Two paths are usually calculated:
  - The critical path, which is the longest time-delay inputs will take to change the output (overall circuit maximum speed)
  - The short path, the shortest time-delay inputs that can start changing the output (in some cases could be the best-case scenario).
  - The propagation delay of a combinational circuit is the sum of the propagation delays through each element on the critical path
  - The contamination delay is the sum of the contamination delays through each element on the short path

 
## Delay Calculation Example

- Find  $t_{pd}$  and  $t_{cd}$  for the following circuit diagram






 
# Delay Calculation Example

- First, we determine critical and short paths



# Delay Calculation Example

    

$$\triangleright t_{pd} = 2 \times t_{pd\_AND} + t_{pd\_OR}$$


$$\triangleright t_{cd} = t_{cd\_AND}$$

# Time Glitches

- Sometimes the circuit design will cause the output to do multiple transitions before it becomes steady
- Usually that is not an issue as long as we wait until the propagation delay elapse.
 
# Glitch Example



- Analyze the following circuit and determine the output transitioning sequence



		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$


# Glitch Example

 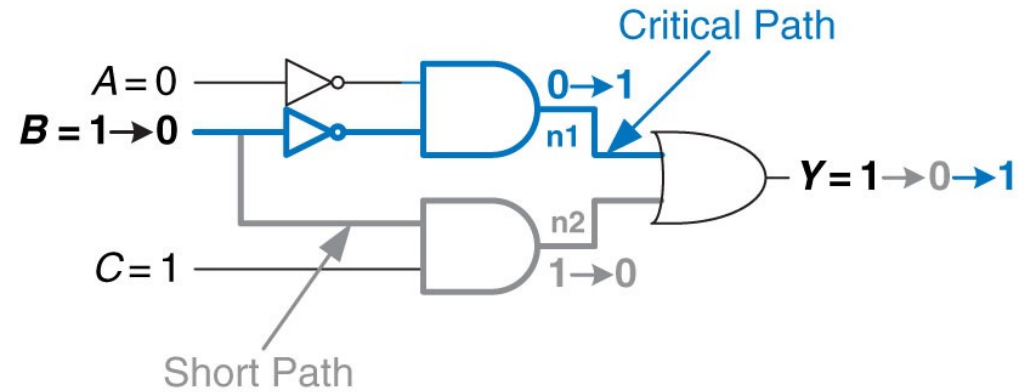


 
# Avoiding Glitches


- From K-Map, a transition from one prime implicant to another could be a potential glitch




$$Y = \bar{A}\bar{B} + BC$$
 
# Avoiding Glitches

- Glitches can be avoided by overlapping prime implicants with additional redundant prime implicants
- This means additional gates added to the circuit.




# Glitch-Free Circuit

 
 
# Sequential Circuits

- Sequential circuits are digital circuits that the output depends on:
  - current input (combinational circuit), and
  - system state: a memory device to preserve the output value



# Example

➤ What is the key difference between these two locks?



Combinational: output depends only on input



Sequential: output depends on new and previous inputs

# Sequential Circuit Types

- **Sequential circuits are differentiated by times at which:**
  - storage elements observe their inputs, and
  - storage elements change their state
- **Synchronous sequential circuits:**
  - Behavior is defined from knowledge of inputs at discrete instances of time
  - Storage elements observe inputs and can change state only in relation to a timing signal (clock pulses from a clock)
- **Asynchronous sequential circuits:**
  - Behavior is defined from knowledge of inputs at any instant of time
  - Storage elements observe inputs and can change state at any instant of time

# To Do List

➤ Review lecture notes